

This question paper contains 3 printed pages]

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 1622

Unique Paper Code : 222453

C

Name of the Paper : (PHCT-402) Physics—II

Name of the Course : B.Sc. (Hons.) Chemistry/Geology

Semester : IV

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Question No. 1 is compulsory.

Attempt *Five* questions in all taking at least *two* questions from each Section.

I. Attempt *five* questions out of the following :

(a) Prove that :

$$\vec{E} = -\nabla V$$

(b) What is Lorentz force ? Write an expression for the Lorentz force.

(c) Write down Maxwell's equation for free space.

(d) Give the truth table of XNOR gate.

(e) Write 2's complement of $(01001101)_2$.

P.T.O.

- (f) Draw the circuit of half wave rectifier.
- (g) When the emitter current of a transistor changes by 1 mA its collector current changes by 0.955 mA. Calculate α and β .
- (h) Write a short note on continuity equation. 3×5=15

Section A

2. (a) Calculate the electric field of a uniformly charged hollow cylinder using Gauss law. 10
- (b) Derive an expression for electric field due to a dipole at a distance ' r ' along its perpendicular bisector. 5
3. (a) Use Maxwell's equation to obtain the wave equation. How did this equation help in the development of the idea that light is also a form of electromagnetic radiation ? 10
- (b) Show that electromagnetic waves are transverse in nature. 5
4. (a) Distinguish between diamagnetic, paramagnetic and ferromagnetic material. 6
- (b) State the laws of electromagnetic induction and describe experiments you would perform to illustrate the factors which determine the magnitude of induced currents set up in closed circuit. 9

Section B

5. (a) Define stability factor "S". Find the stability factor in CE configuration using base resistor method. 8
- (b) How voltage divider bias method works in CE configuration for good stabilization. 7

6. What is rectification ? Draw and explain the working of full wave rectifier and obtain the expression for efficiency and ripple factor. 15
7. (a) Write the truth table for a half subtractor and draw its circuit diagram using NAND gates. 7
- (b) Prove that : 4
- $$(A + B) (A + \bar{B}) (\bar{A} + C) = AC.$$
- (c) Convert $(3827)_{10}$ into binary and octal numbers. 4