

This question paper contains 4 printed pages]

Your Roll No. ....

1973

**B.Sc. (Hons.) (Computer Science)/I Sem. C**

Paper 104—DIGITAL ELECTRONICS

(Admissions of 2001 and onwards)

Time : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt *all* questions.

Part of a question must be answered together.

1. (a) Convert the following : 2

(i)  $(129.375)_{10} = ( )_2$

(ii)  $(3A7B)_{16} = ( )_8$

(b) What is radix (base) that satisfies the following equation : 2

$$(53)_r + (120)_r = (213)_r$$

P.T.O.

- (c) Express the following function in both the canonical forms : 2

$$f = (W.X' + Y.Z') (W'.Z + X.Y')$$

- (d) Implement a full adder using 3 to 8 decoder. 2

- (e) What is race around condition in JK flip-flop and how it can be removed ? 2

- (f) Convert a J-K flip-flop into a D flip-flop as well as T flip-flop. 2

- (g) Differentiate between static and dynamic RAM. 1

- (h) Subtract  $(125)_{10}$  from  $(200)_{10}$  using complement method. 2

2. (a) Simplify the following function in SOP form and realize it using universal gate : 7

$$F = \sum m(0, 2, 3, 10, 12, 16, 17, 18, 21, 26, 27) \\ + d(11, 13, 19, 20)$$

- (b) Reduce the following expression using Boolean algebra : 5

$$F = (W.X + W.Y') (W + X) + W.X. (X' + Y')$$

3. (a) Design a 4-bit BCD adder circuit using two 4-bit binary adders and a correction detector circuit. 7
- (b) Implement following function using  $4 \times 1$  MUX and external gates : 5

$$F = \pi(0, 2, 3, 8, 9, 13, 15).$$

4. (a) Design a sequential circuit with two JK flip-flop A and B and two inputs E and x. If  $E = 1$ , the circuit remains in the same state regardless of the value of x. When  $E = 0$  and  $x = 0$ , the circuit goes through the state transition from 00 to 01 to 10 to 11, back to 00, and repeats. When  $E = 0$  and  $x = 1$ , the circuit goes through the state transition from 00 to 11 to 10 to 01 and back to 00 and repeats. 7
- (b) An XY flip-flop has 4 operations set to 1, complement, no change and set to 0 when X and Y inputs are 00, 01, 10 and 11 respectively. Tabulate its characteristic table and excitation table. Derive its characteristic equation. 5

5. (a) Design a synchronous counter using T flip-flop that goes through states : 7.

$$0 \rightarrow 3 \rightarrow 5 \rightarrow 6 \rightarrow 0$$

- (b) Construct a  $32 \times 1$  MUX using  $8 \times 1$  MUX and a  $4 \times 1$  MUX. 5
6. (a) Draw and explain an architecture of  $16 \times 8$  ROM. 6
- (b) A certain memory stores 8K 16-bit words. How many data input and output lines does it have ? How many address lines does it have ? What is its bit capacity ? 6