

This question paper contains 4 printed pages.]

Your Roll No.

1396

A

B.Sc. (Hons.)/I

ELECTRONIC SCIENCE—Paper 1.5 (V)

(Network Analysis and Linear Active Circuits)

Time : 3 Hours


Maximum Marks : 38

*(Write your Roll No. on the top immediately
on receipt of this question paper.)*

*Attempt five questions in all including
Question No. 1 which is compulsory.*

Non Programmable Scientific calculator is allowed.

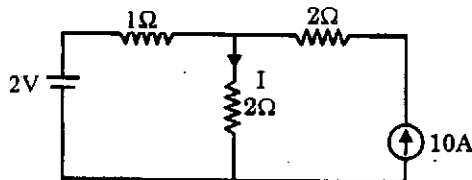
1. Attempt any **five** 2 × 5
(a) Determine the current **I** in the following circuit.




- (b) Three equal resistance of 3Ω are connected in star network. What is the resistance in one of the arms in the equivalent delta circuit.
- (c) Two identical sections of the π network are connected in parallel. The Y-parameters of the network are : $Y_{11} = 3\mathfrak{U}$, $Y_{12} = Y_{21} = -2\mathfrak{U}$, $Y_{22} = 3\mathfrak{U}$. Determine the overall Y-parameters of resulting network.

[P.T.O.]

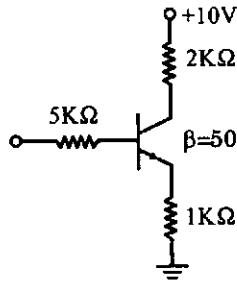
- (d) Find the operating point of the following circuit.



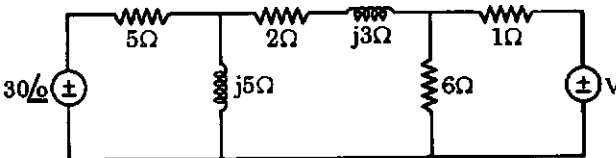
- (e) Define Peak Inverse Voltage of a diode. What is the PIV rating of a diode in case of Bridge rectifier in comparison to CT-FWR if turns ratio of the transformer used is same in both rectifiers.
- (f) What type of feedback is preferred for designing of a oscillator and why ?
2. (a) In the following network, determine the voltage V which result in zero current through $(2 + j3) \Omega$ 4



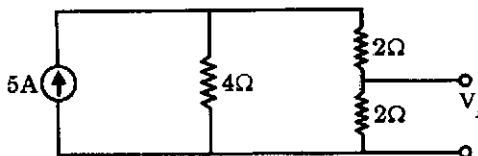
- (b) Verify reciprocity theorem by computing V_x . 3



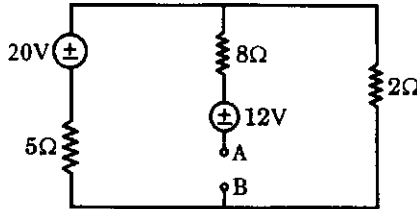3. (a) Find the Norton's equivalent of the following circuit across AB. 4



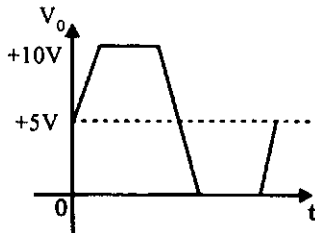- (b) Design a circuit to generate an output wave form as shown in figure below for a 20V peak to peak sinusoidal input signal 3



4. (a) Derive the exact expression of ripple factor for a full wave bridge rectifier with capacitor filter. 5
- (b) Define Transformer Utility Factor and find its value for a full wave rectifier. 2
5. (a) Define various stability factors. Derive the expression for variation of collector current with respect to β in self bias circuit. 5
- (b) Explain for a given spread in the value of β , a high β circuit will be more stable. 2

6. (a) What is the advantage and disadvantage of using capacitive coupling in a multi-stage amplifier. 1
- (b) Draw frequency response curve of a 2-stage RC coupled amplifier and derive the expression for its mid-frequency gain. 4
- (c) Explain why the gain drops in the low-frequency and high-frequency region. 2
7. (a) For an amplifier with following specifications gain $(A) = 100$, $R_i = 10 \text{ k}\Omega$, $R_o = 1 \text{ k}\Omega$. 3
if a negative feedback of 25% of voltage series type is introduced, what will be the corresponding change in the given specifications.
- (b) Draw the circuit diagram of Colpitt oscillator and derive expression for its frequency of oscillation. 4