

[This question paper contains 6 printed pages.]

5993

Your Roll No. ....

**B.Sc. (H) ELECTRONICS / 1st Sem.**

**B**

Paper – ELHT-103

Networks Analysis

(Admissions of 2010 and onwards)

Time : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately  
on receipt of this question paper.)

Attempt Five questions in all  
including Q. No. 1 which is compulsory.  
Scientific calculator is allowed.

1. (i) Sketch the dual of the network given in Fig. 1.

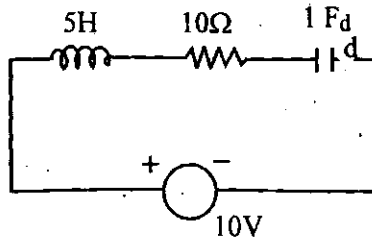


Fig. 1

- (ii) Solve the current through  $3\Omega$  resistor using Millman's theorem for Fig. 2.

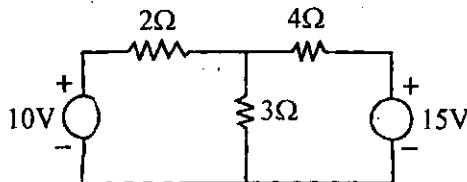


Fig. 2

P.T.O.

- (iii) A  $5 \mu\text{F}$  capacitor with an initial voltage of  $4\text{V}$  is connected to a parallel combination of  $3 \text{K}\Omega$  & a  $6 \text{K}\Omega$  resistor (Fig. 3). Find the transient current in the  $6 \text{K}\Omega$  resistor

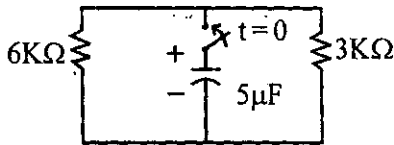


Fig. 3

- (iv) Design a passive band pass filter for the frequencies from  $1 \text{KHz} - 20 \text{KHz}$  using low pass filter and high pass filter.
- (v) Write expression for the impedance of a parallel RLC network. What is the impedance at resonant frequency? (5×3)

2. (a) Determine  $I_b$  in the circuit of Fig. 4

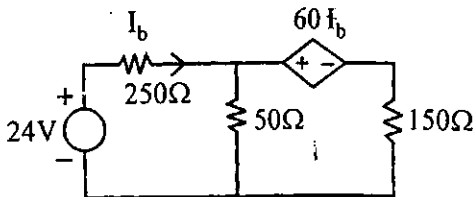


Fig. 4

- (b) Find the current through  $1\Omega$  resistor using Thevenin's theorem. (Fig. 5)

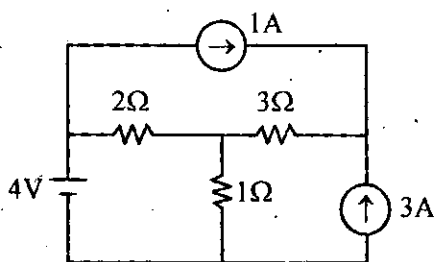


Fig. 5

(5+10)

3. (a) For the circuit of Fig. 6. Find  $i_0$  for  $t > 0$ .

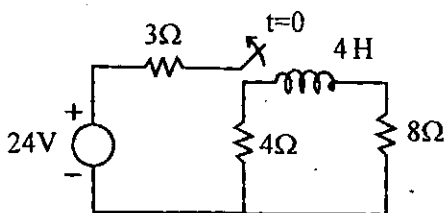


Fig. 6

- (b) Assuming that the switch in Fig. 7 has been in position A for a long time and is moved to position B at  $t = 0$ . Find  $v_0(t)$  for  $t > 0$ .

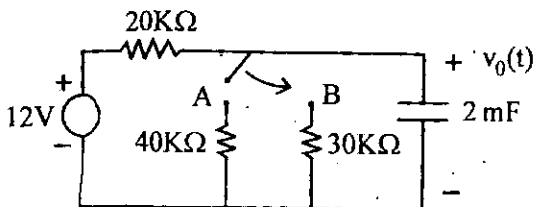


Fig. 7

(7+8)

P.T.O.

4. (a) Find expressions for RMS and average values for a full wave rectified waveform (sinusoidal).
- (b) For a voltage source feeding a load of  $15\Omega$  &  $-10j\Omega$  through a transmission line of  $(4+2j)\Omega$  impedance, find the real power, reactive power and apparent power. (Fig. 8)

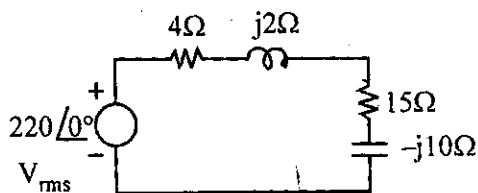


Fig. 8

- (c) Obtain the elements of the series circuit corresponding to the voltage-current-phasor diagram (Fig. 9), if the frequency is 21.2 KHz.

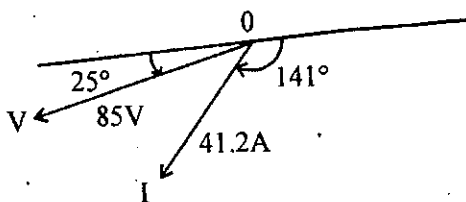


Fig. 9

(8+3+4)

5. (a) Obtain the Norton equivalent of the network of Fig. 10 at terminals xy

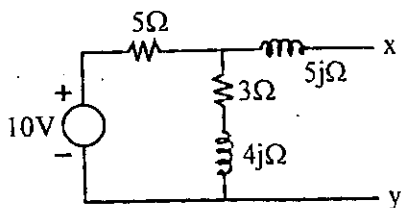


Fig. 10

- (b) Find the current through the  $1\Omega$  resistor using Thevenin Theorem (Fig. 11)

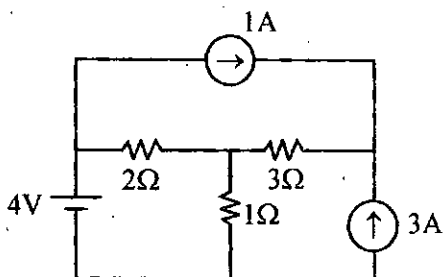


Fig. 11

- (c) Obtain the voltage  $v_L$  across the inductor in Fig. 12.

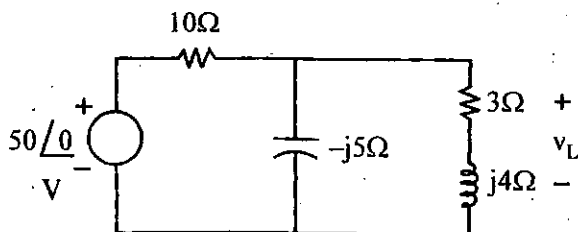


Fig. 12

(5×3)

6. (a) For a series RLC circuit with  $R = 100\Omega$ ,  $L = 0.5H$  &  $C = 0.4\mu F$ , find the resonant frequency. Also obtain the half power frequencies & bandwidth.
- (b) A low pass RC filter has  $R = 5K\Omega$ . What value of  $C$  results in a gain of 0.90 at 8 KHz? Obtain the voltage gain at 12 KHz. (10+5)

P.T.O.

7. (a) Find the Y-parameters of the two-port network of Fig. 13.

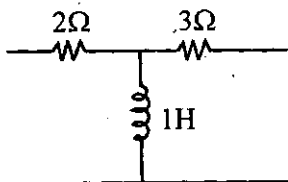


Fig. 13

- (b) Given the Y-parameters of a network

$$Y = \begin{pmatrix} \frac{1}{6} & \frac{1}{6} \\ -\frac{1}{12} & \frac{5}{12} \end{pmatrix}$$

Find its Z parameters and draw its equivalent Z model.

- (c) Find the h-parameters of the given network (Fig. 14).

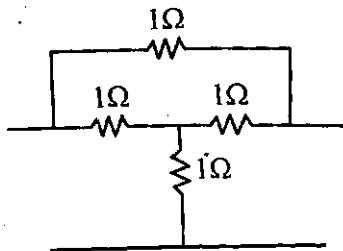


Fig. 14

(5×3)