

[This question paper contains 4 printed pages.]

Sr. No. of Question Paper : 8733

C

Roll No.....

Unique Paper Code : 251104

Name of the Paper : ELHT-103 : Network Analysis

Name of the Course : B.Sc. (Hons.) Electronics – Part I

Duration : 3 Hours


Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)


**Instructions for Candidates**

Attempt five questions in all. Question No. 1 is compulsory.  
Use of Non-programmable Scientific calculators is permitted.

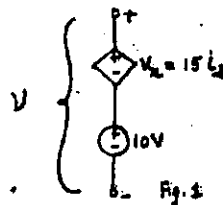
- Q1. (a) Obtain the voltage  $v$  in the branch shown in Fig.1 for  
(i)  $i_2 = 1A$ , (ii)  $i_2 = -2A$ , (iii)  $i_2 = 0A$



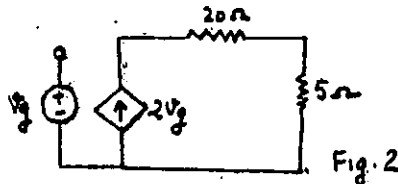
- (b) State the Millman's Theorem.  
(c) Calculate the energy dissipated in the  $5\Omega$  resistor of Fig.2 during the interval  $0 < t < 5ms$ , if  $v_g = 5000t$  (V).



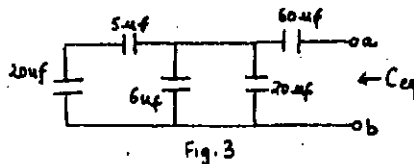- (d) Find the equivalent capacitance seen between terminals a and b of the circuit in Fig.3.



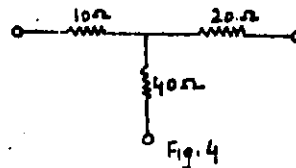- (e) Transform the T network shown in Fig.4 into its equivalent  $\Pi$  network.




(3x5)  
P.T.O.


Q2. (a) A series circuit with  $R = 2\Omega$ ,  $L = 2\text{mH}$  and  $C = 500\mu\text{F}$  has a current which increases linearly from zero to  $10\text{A}$  in the interval  $0 \leq t \leq 1\text{ms}$ , remains at  $10\text{A}$  for  $1\text{ms} \leq t \leq 2\text{ms}$ , and decreases linearly from  $10\text{A}$  at  $t = 2\text{ms}$  to zero at  $t = 3\text{ms}$ . Sketch  $v_R$ ,  $v_L$  and  $v_C$ .

(b) (i) Obtain the equivalent resistance for the circuit shown in Fig.5.

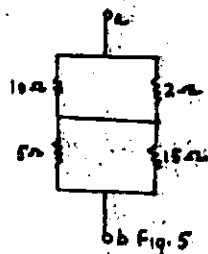(ii) With a constant voltage applied to terminal ab, which resistor absorbs the greatest power?



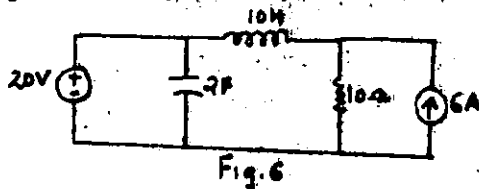
(c) Explain the principle of Duality. Obtain the dual of the network shown in Fig.6.



(5, 4, 6)


Q3. (a) State and Prove the Norton's theorem.

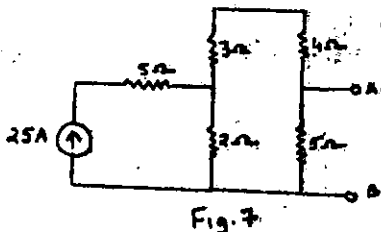(b) Determine Norton's equivalent, for the circuit given in Fig.7, across AB.




Contd.

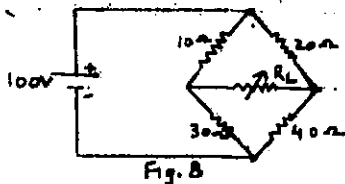(c) Find the maximum power delivered to  $R_L$  in Fig.8.




(5, 5, 5)

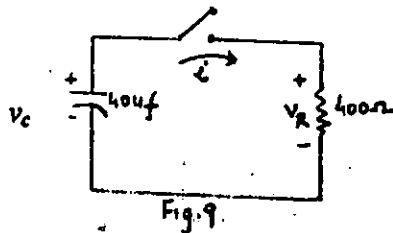
Q4. (a) At  $t = 0^-$ , just before the switch is closed in Fig.9,  $v_C = 100\text{V}$ . Obtain the current and charge transients. Also obtain the power and energy in the resistor, and compare the latter with the initial energy stored in the capacitor.



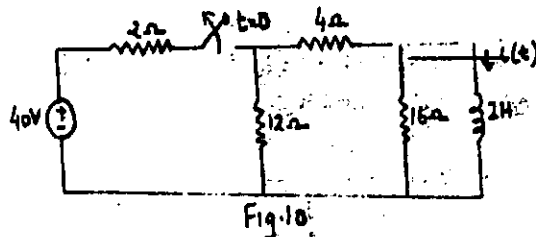- (b) The switch in the circuit of Fig. 10 has been closed for a long time. At  $t = 0$ , the switch is opened. Calculate  $i(t)$  for  $t > 0$ .




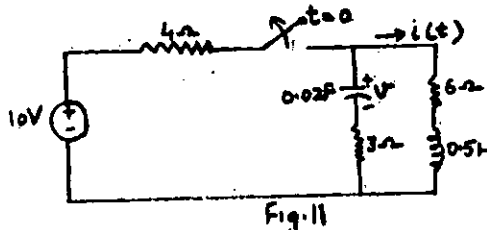- (c) Find  $i(t)$  in the circuit in Fig. 11. Assume that the circuit has reached steady state at  $t = 0^-$ .




(5, 4, 6)

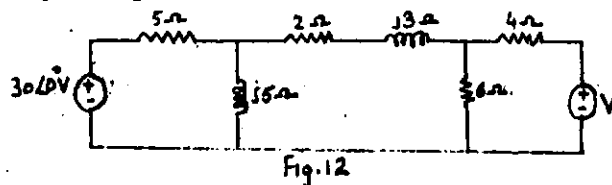- Q5. (a) In the network of Fig. 12, determine the voltage  $V$  which results in a zero current through the  $2 + j3\Omega$  impedance.




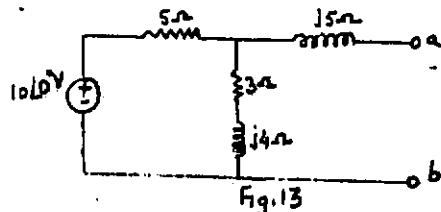- (b) For the network of Fig. 13, obtain the Norton's equivalent circuit.




- (c) Find the current  $I_x$  through the inductor in Fig. 14, by first obtaining the transfer impedance. Let  $V = 10\angle 30^\circ$  V.

P.T.O.

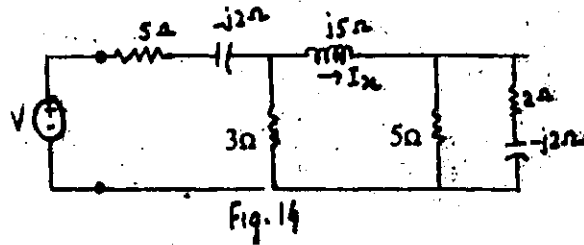


(5, 5, 5)

- Q6. (a) Derive the expression for the Voltage Transfer function,  $H_v(\omega)$ , of RL High-Pass filter and plot its magnitude.  
 (b) Find L in the High-Pass circuit shown in Fig.15 if  $|H_v(\omega)| = 0.50$  at a frequency of 50 MHz. Also find half-power frequency.

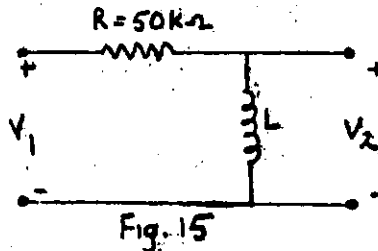


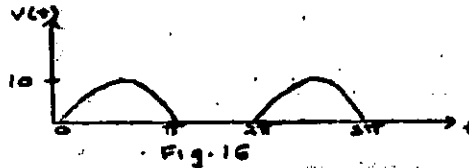- (c) Find the rms value and the amount of average power dissipated in a  $10\Omega$  resistor if the voltage across it is a half-wave rectified sine wave as shown in Fig.16.



(5, 5, 5)

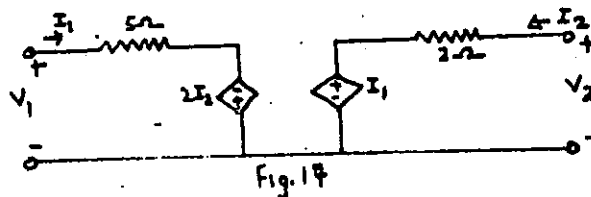- Q7. (a) Derive the conversion formulae for obtaining the Y parameters from the Z parameters.  
 (b) Find the Z parameters of the circuit given in Fig.17. Also obtain the Y parameters using the Z parameters



- (c) If the transfer impedances of a two port linear network are equal, what does it indicate? Explain.

(700)\*\*\*\*