

This question paper contains 7 printed pages]

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 6444

Unique Paper Code : 251104

D

Name of the Paper : Network Analysis (ELHT-103)

Name of the Course : B.Sc. (Hons.) Electronics

Semester : I

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt Five questions in all.

Question No. 1 is compulsory.

Use of non-programmable scientific calculator is permitted.

1. (a) An equivalent circuit has the Norton current $12 \angle 0^\circ$ A and the Thevenin impedance is $8-6j \Omega$. What is the maximum average power that can be transferred to the load ?
- (b) Determine the r.m.s. value of the voltage for the periodic waveform shown in Fig. 1a below :

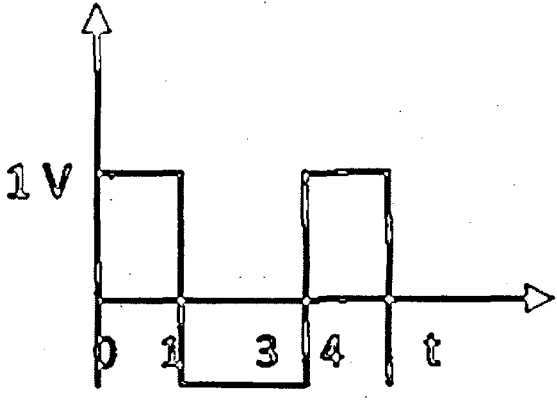


Fig. 1a

- (c) In a low pass RC filter with cut-off frequency 1 kHz the capacitor C is replaced by $4C$, and now the output is taken across the resistance. What is the cut-off frequency of this filter? Sketch the frequency response of this system with capacitance of $4C$.
- (d) Draw the Dual Circuit for the given circuit of Fig. 1b.

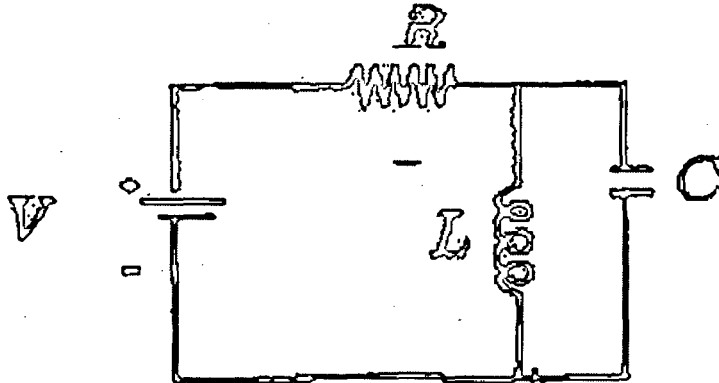


Fig. 1b

- (e) Define the hybrid parameters for a two-port network. Identify each of these parameters specifically (by name also). 3×5=15
2. (a) Loop currents are shown in the network of Fig. 2a. Write the matrix equation and solve for the three currents. 8

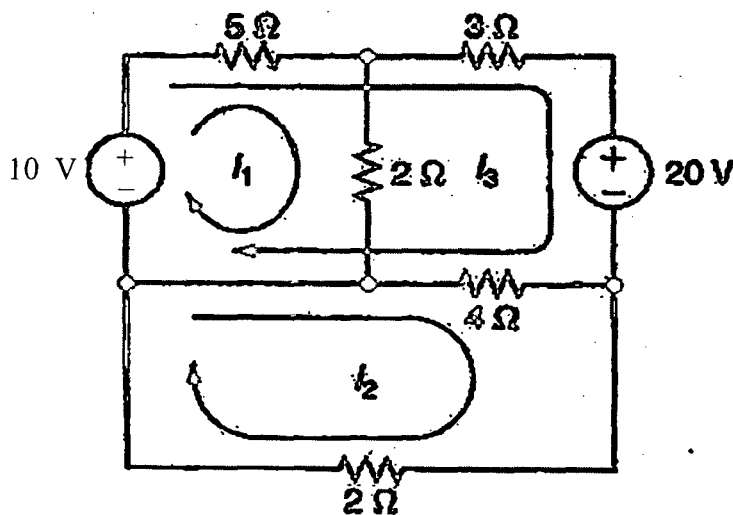


Fig. 2a

(b) In the network shown in Fig. 3a, find the current in the $10\ \Omega$ resistor. 7

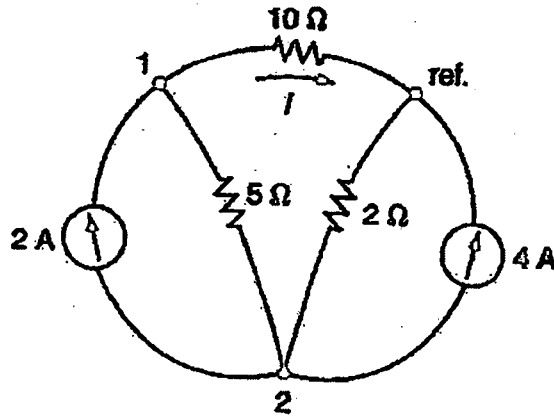


Fig. 2b

3. (a) State and prove the Thevenin's theorem. 7

(b) For the bridge network in Fig. 3, find R_{ab} and i . 8

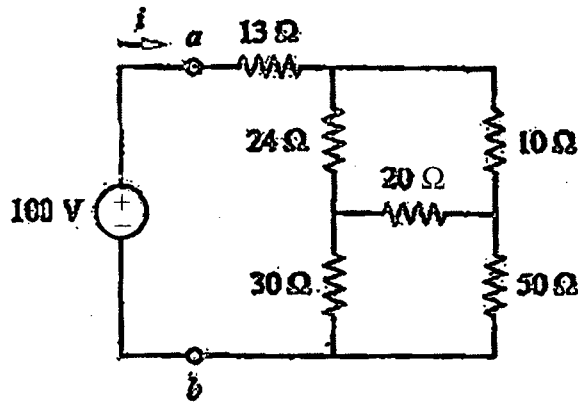


Fig. 3

4. (a) The switch in the circuit shown in Fig. 4a is closed at $t = 0$, at which moment the capacitor has charge $Q_0 = 500 \mu\text{C}$, with the polarity indicated. Obtain i and q , for $t > 0$, and sketch the graph of q . 7

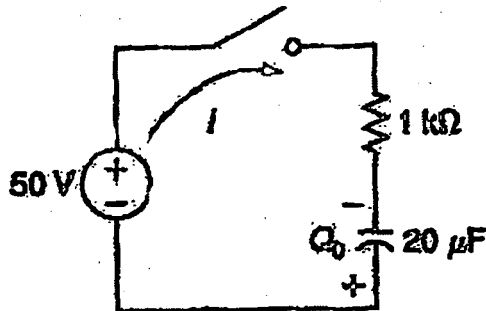


Fig. 4a

- (b) A series RLC circuit with $R = 200 \Omega$, $L = 0.10 \text{ H}$, and $C = 1 \mu\text{F}$, has an initial charge on the capacitor of $Q_0 = 2.67 \times 10^{-3} \text{ C}$. A switch is closed at $t = 0$, allowing the capacitor to discharge. Obtain the current transient. (See Fig. 4b). 8

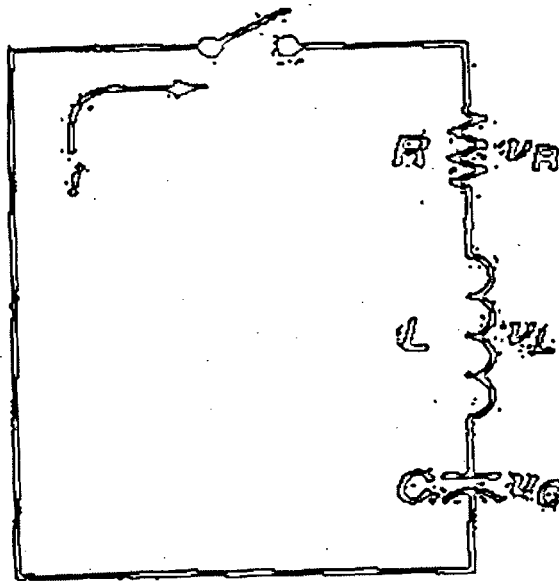


Fig. 4b

5. (a) Find the input impedance of the circuit in Fig. 5a. Assume that the circuit operates at $\omega = 50$ rad/s. 7

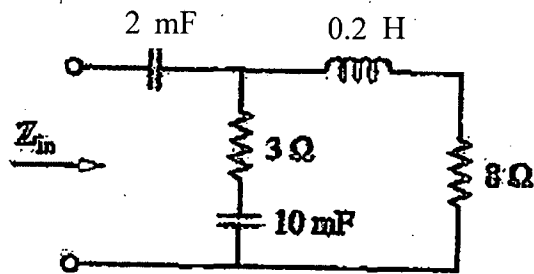


Fig. 5a

- (b) Replace the active network in Fig. 5b at terminal ab with a Norton equivalent. 8

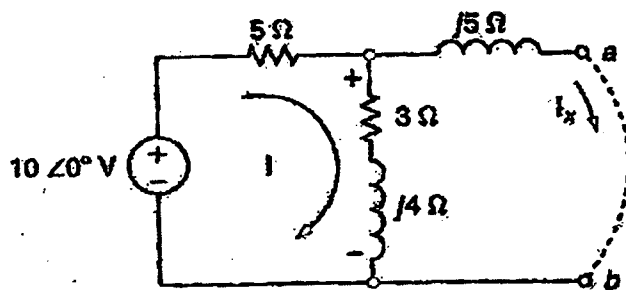


Fig. 5b

6. (a) Calculate the power factor of the entire circuit of Fig. 6a as seen by the source. What is the average power applied by the source ? 8

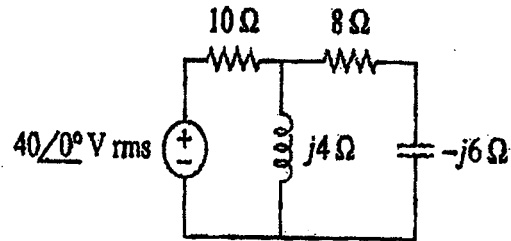


Fig. 6a

- (b) Obtain the voltage transfer function $H_v(\omega)$ under no load condition for the open circuit shown in Fig. 6b. At what frequency, in hertz, does $|H_v(\omega)| = \frac{1}{\sqrt{2}}$ if $C_2 = 10$ nF ? 7

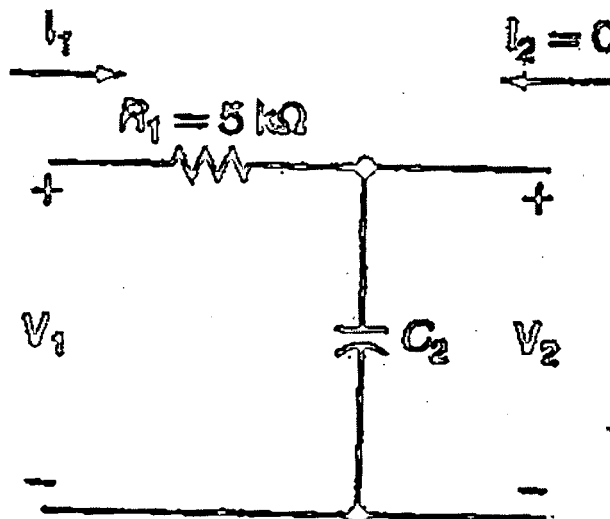


Fig. 6b

7. (a) Determine the Z parameters for the two-port network shown in Fig. 7a shown below. 7

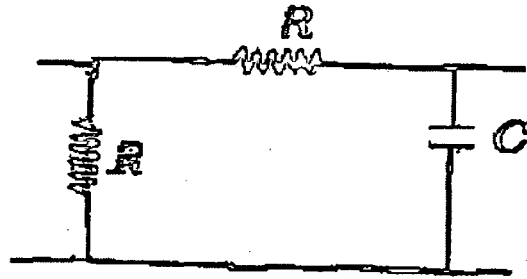


Fig. 7a

- (b) Identify the condition for a network to be reciprocal in terms of its Z parameters. Given the Y-parameters of a two-port network identify its Z-parameters. 8

$$\begin{pmatrix} 6 & 4 \\ 4 & 7 \end{pmatrix} \Omega^{-1}$$