

Sl. No. of Ques. Paper : 944

G

Unique Paper Code : 251104

Name of Paper : Network Analysis : ELHT-103

Name of Course : B.Sc. (Hons.) Electronics

Semester : I

Duration : 3 hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt five questions in all.

Question No. 1 is compulsory.

All questions carry equal marks.

Use of non-programmable scientific calculator is allowed.

1. Attempt all parts of this question:

(a) How to implement:

(i) 10 A current source if two 5 A current sources are available .

(ii) 10 V voltage source if two 5 V voltage sources are available.

(iii) 150  $\mu$ F capacitor if only 100  $\mu$ F capacitors are available.


3

(b) What is power factor? Explain its significance.

3

(c) Find the equivalent inductance between terminals 1 and 2:

3

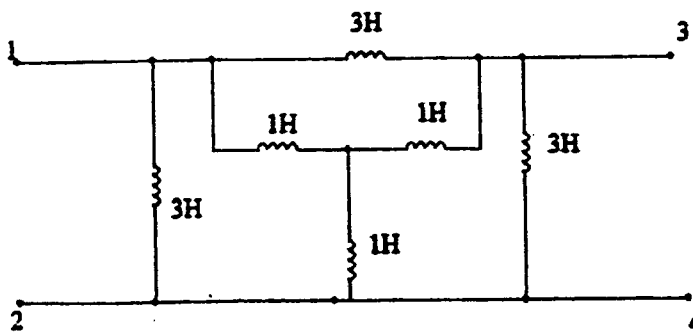


(d) In a series RL circuit having  $R=2 \Omega$  ,  $L=10$  H with the DC voltage of 100 volts find the value of current after 5 ms of switching ON.

3


(e) Find the Y parameters for the given circuit.

3


P. T. O.

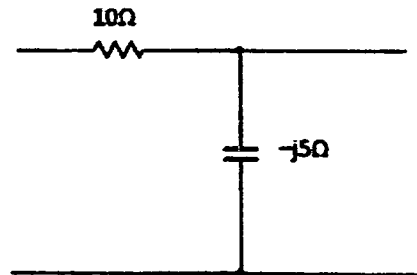

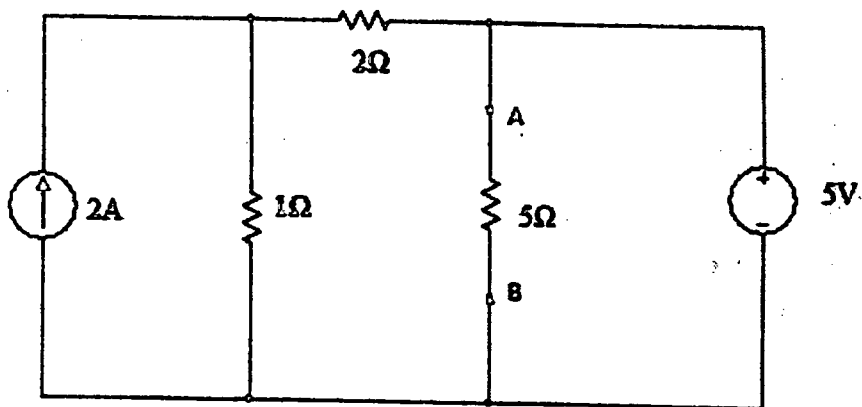
2. (a) Find the Thevenin equivalent of the given circuit. Determine the current through  $5\ \Omega$  load resistor. Justify that the Thevenin equivalent circuit is equivalent to an ideal voltage source. 5



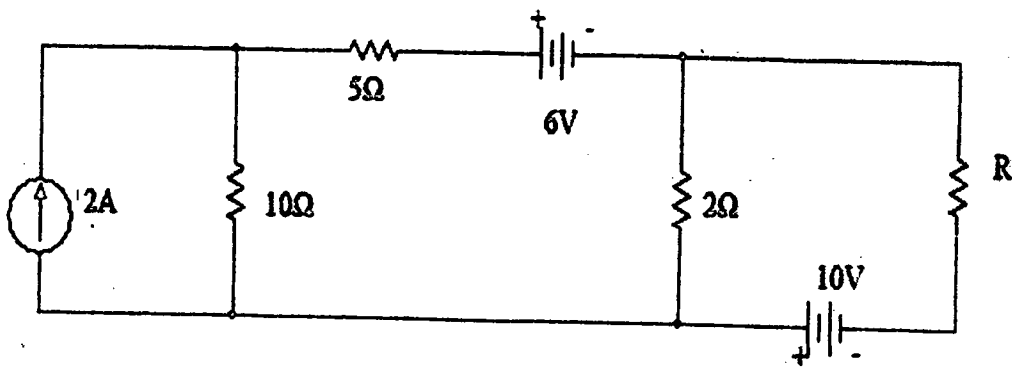
- (b) Find  $R$  to have maximum power transfer in the given circuit. Also obtain the amount of maximum power transferred. 5



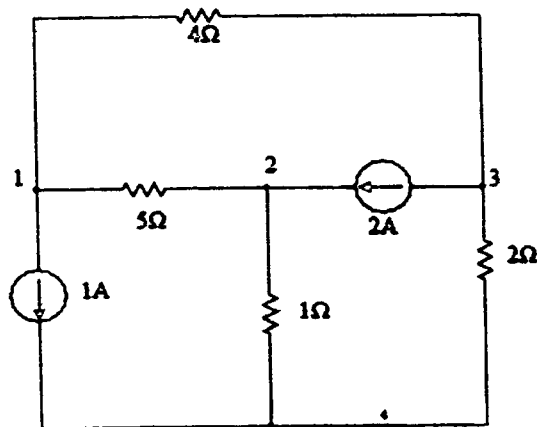
- (c) Find the current through  $5\ \Omega$  resistor using nodal analysis. 5



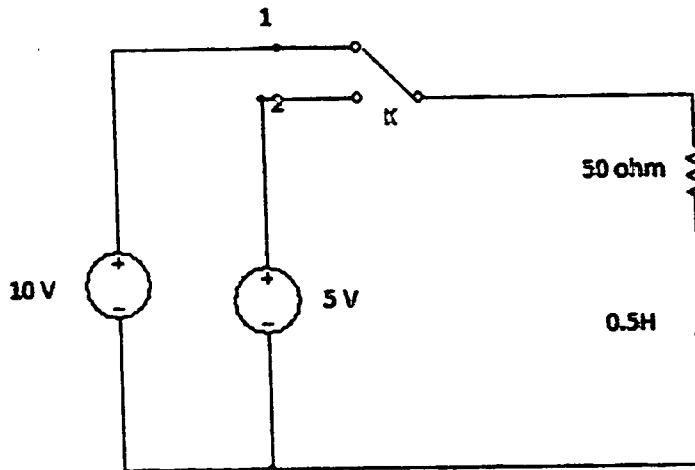3. (a) In the given circuit switch is in position 1 for sufficient time to establish the steady state and then moved to switch 2. Find the current in both the conditions and sketch the transient. 6




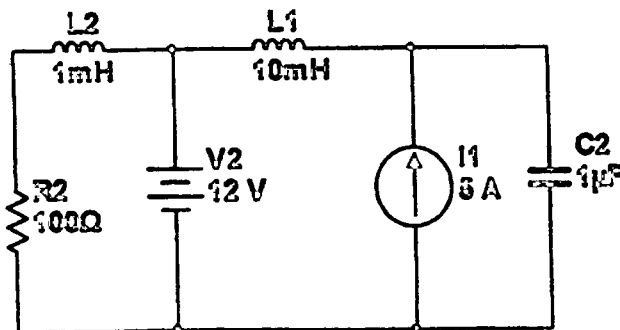- (b) What is duality? Obtain the dual of the circuit given below. 5




- (c) A current  $i = I_m \sin \omega t$  passes through a series RC circuit. Determine the voltage across each element and draw the voltage and current waveforms (properly depicting the relative phase difference) for each element. 4

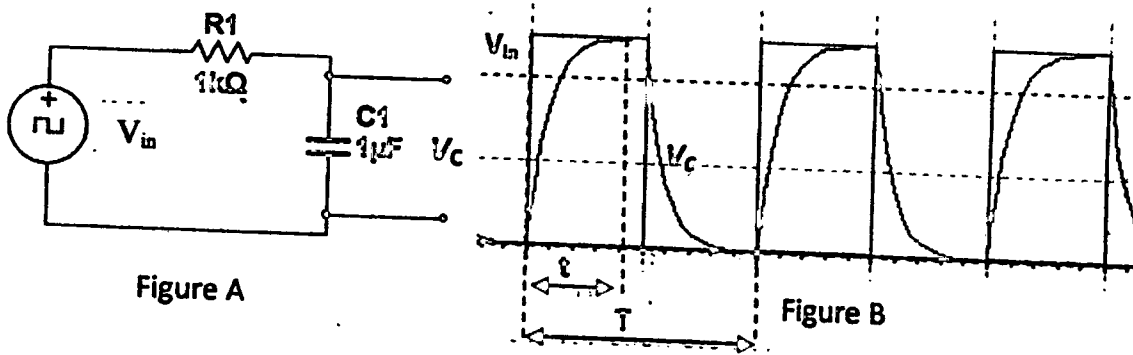
4. (a) Find whether the parallel RLC circuit with  $R=200 \Omega$ ,  $L=0.28 \text{ H}$ ,  $C=3.57 \mu\text{F}$  and initial capacitor voltage of  $50 \text{ V}$  would oscillate or not. Obtain the voltage function for  $t \geq 0$ . 6
- (b) The input and output waveforms for the circuit given in figure A are shown in figure B. Find:
- (i) Time  $t$  for the capacitor voltage almost reaching the input maximum. 6
  - (ii) The bandwidth of pass band for the filter formed by the given series RC circuit. 3



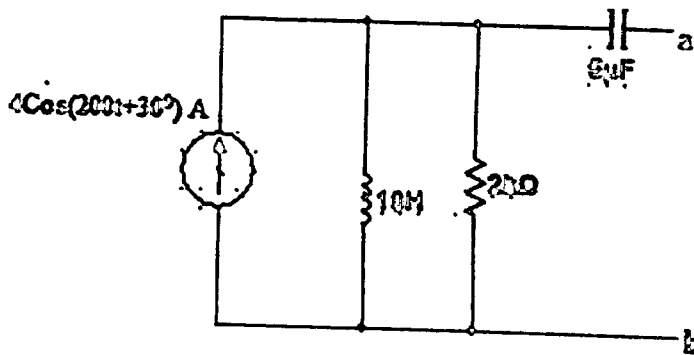- (c) (i) For the circuit in figure A, explain the effect of increasing the input frequency on the capacitor voltage for the following 3 cases: 6  
 $t \ll T/2$ ;  $t = T/2$ ;  $t \gg T/2$
- (ii) In which of the above cases does the circuit act as an integrator? 6
5. (a) Obtain Norton's equivalent of the circuit depicted in figure below: 5



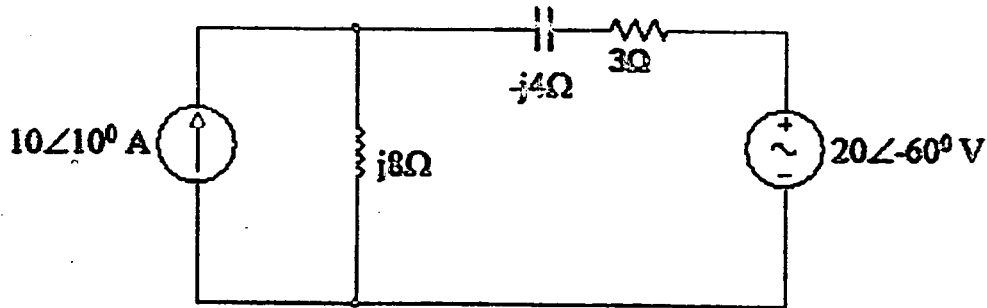- (b) Using Superposition principle, find current in  $3-j4 \Omega$  impedance in the circuit given below: 5



(c) For a load,  $V_{rms} = 110\angle 85^\circ$  V,  $I_{rms} = 0.4\angle 15^\circ$  A. Determine:

- (i) the complex and apparent powers
- (ii) the real and reactive powers
- (iii) the power factor.

5

6. (a) A circuit consisting of a coil with inductance 10 mH and resistance 20  $\Omega$  is connected in series with a capacitor and generator with an r.m.s. voltage of 120 V. Find:

- (i) the value of capacitance that will cause the circuit to be in resonance at 15 kHz.
- (ii) the current through the coil at resonance
- (iii) the Q and bandwidth of the circuit.

5


(b) Design an RC low pass filter that uses  $C = 0.1 \mu\text{F}$  and has cutoff frequency 15 kHz.

- (i) If  $V_{in} = 10$  V then find out the output voltage at twice the cutoff frequency
- (ii) Determine the frequency at which  $V_{out}$  is  $0.5V_{in}$

5


(c) The two impedances  $Z_1$  and  $Z_2$  shown below are in series with voltage source  $V_s = 100\angle 0^\circ$  V. Find the voltage across each impedance and draw the voltage phasor diagram showing  $V_s$  as a resultant of  $V_1$  and  $V_2$ .

5

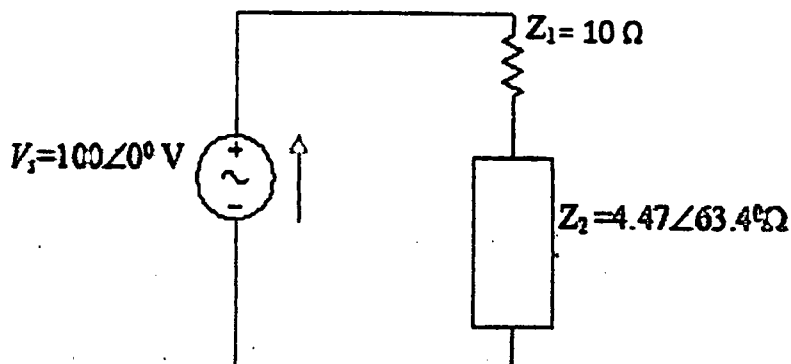

7. (a) Find  $Z$  parameters for the network shown in the figure.

6

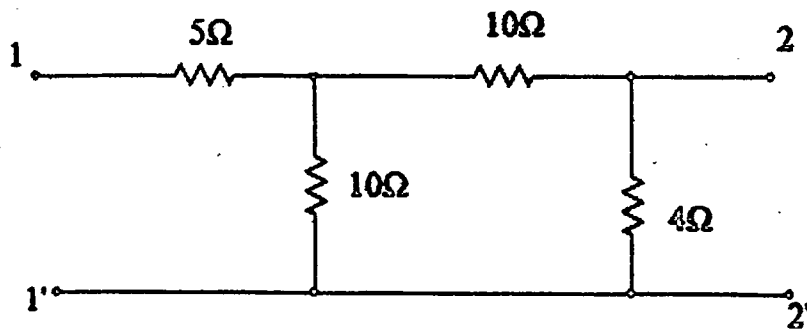

- (b) Derive the expression for  $h$  parameters from  $Z$  parameters. Show that  $h$  parameter does not exist if  $Z_{22}$  is zero. 5
- (c) Draw the  $h$  equivalent for the circuit shown in part (a) after finding the  $h$  parameters using the expressions derived in part (b). 4