

This question paper contains 4 printed pages.]

Your Roll No. ....

**1402**

**B.Sc. (Hons.) / II A**

**ELECTRONIC SCIENCE – Paper 2.4 (XI)**

**(Instrumentation)**

**Time : 3 Hours**


**Maximum Marks : 38**

*(Write your Roll No. on the top immediately on receipt of this question paper.)*

Attempt five questions in all, including  
Question No. 1, which is compulsory.


1. (a) In a CRO, why and where are delay lines used ? 2
- (b) What are the characteristics of a regulated power supply ? 2
- (c) What is the difference between a square wave generator and a pulse generator ? 2
- (d) What is Wagner ground connection ? Where is it used ? 2

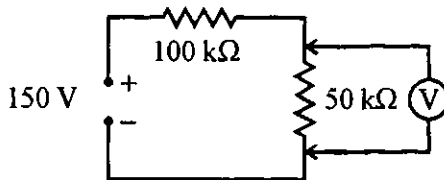- (e) It is desired to measure the voltage across the  $50\text{ k}\Omega$  resistor in the given circuit. Two voltmeters are available for this measurement : Voltmeter 1 with a sensitivity of  $1,000\ \Omega/\text{V}$  and Voltmeter 2 with a sensitivity of  $20,000\ \Omega/\text{V}$ . Both meters are used on their  $50\text{ V}$  range. Calculate the reading of each meter. 2



2. (a) Draw the block diagram of a general purpose CRO briefly explaining function of each block. 4
- (b) Draw Lissajous patterns (i) when a 3 KHz frequency signal is connected to vertical and 2 KHz frequency signal is connected to horizontal deflection plates (ii) when a 3 KHz frequency signal is connected to vertical and 5 KHz frequency signal is connected to horizontal deflection plates. 3

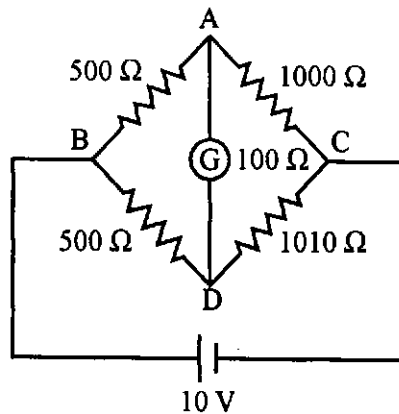3. (a) If the sensitivity of galvanometer in the given circuit is  $10 \text{ mm}/\mu\text{A}$ , determine its deflection. 4



- (b) How is Hay bridge different from Maxwell bridge? How do you use it for measuring high Q coils? 3
4. (a) How will you measure the Q of low impedance components? 4
- (b) A coil with a resistance of  $10 \Omega$  is connected in the "direct measurement" mode of a Q meter. Resonance occurs when the oscillator frequency is  $1 \text{ MHz}$  and the resonating capacitor set at  $65 \text{ pf}$ . Find the percentage error introduced in the calculated value of Q by the  $0.02 \Omega$  insertion resistance. 3

5. (a) Give the elements of a standard signal generator. How is it different from a function generator? 4
- (b) Explain the working of Staircase-ramp Digital Voltmeter. 3
6. (a) Explain period and ratio measurement mode of Universal Counter. 4
- (b) Suggest three ways in which you can obtain maximum accuracy in a universal counter. 3
7. (a) Explain the working of IC723 as voltage regulator. 4
- (b) How are shunt regulators different from series regulators? 3
-