

This question paper contains 3 printed pages]

Roll No. 

--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 6887

Unique Paper Code : 222461

**D**

Name of the Paper : Digital Electronics (ELPT-404)

Name of the Course : B.Sc. Physical Sciences (Electronics)

Semester : IV

Duration : 3 Hours

Maximum Marks : 75

*(Write your Roll No. on the top immediately on receipt of this question paper.)*

Attempt any Five questions.

All questions carry equal marks.

1. (a) Subtract 01101 from 11011 using the 1's complement method. 5
- (b) Convert the binary number 1100 to its Gray-Code equivalent. 5
- (c)  $(5AB.1C)_{16} = (?)_{10}$  2.5
- (d)  $(19)_{10} = (?)_8$ . 2.5
2. (a) Draw the circuit diagram of XNOR gate using NAND gates and give its truth table. 5
- (b) Explain with suitable diagram, the working of TTL circuits. 5
- (c) What is AND-OR network for,  $Y = A'B'C + ABC' + AB'C + ABC$  after simplification? 5

P.T.O.

3. (a) Develop the Product-Of-Sum expression for  $F_1$ ,  $F_2$  and  $F_3$  given in the table : 7

A	B	C	$F_1$	$F_2$	$F_3$
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	1
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	1
1	1	1	1	0	1

- (b) Simplify the following function and design a circuit diagram with NAND gate : 8

$$F(A, B, C, D) = \sum_m(0, 4, 5, 8, 9, 10, 11, 12, 13, 14, 15).$$

4. (a) What is Demultiplexer ? Explain its operating principle. Discuss the 1-line-to-4-line Demultiplexer. 8
- (b) What is Decoder ? Explain the Decoder for BCD to Decimal with circuit diagram. 7
5. (a) Draw the circuit diagram and truth table of Half Subtractor. 5
- (b) Explain and draw the circuit diagram of Full Adder with truth table. 5
- (c) Show that : 5

$$ABC + AB'C + ABC' = A(B + C).$$

6. (a) What is D-Flip Flop ? Draw its logic circuit and explain the operation. 8
- (b) Draw and explain the logic circuit of the 4-bit Asynchronous Ripple Counter and design its waveform. 7
7. (a) Draw the waveform to shift the number 0100 into the Shift register, Serial In-Serial Out and explain its operation. 10
- (b) For the 5-bits resistive divider, determine the following :
- (i) The weight assigned to the LSB. 1
- (ii) The weight assigned to second and third LSB. 1.5
- (iii) The output voltage for a digital input of 1101. Assume  $0 = 0 \text{ V}$  and  $1 = +10 \text{ V}$ . 2.5
8. Write short notes on any *three* : 5+5+5
- (i) RAM
- (ii) PROM
- (iii) CMOS
- (iv) D/A converter.