

This question paper contains 3 printed pages.]

Your Roll No.

1412

A

B.Sc. (Hons.)/III
ELECTRONICS – Paper – 3.7(XXI)
(Power Electronics)

Time : 3 Hours

Maximum Marks : 38


(Write your Roll No. on the top immediately
on receipt of this question paper.)

*Attempt Five questions in all, including
Question No. 1 which is compulsory.*

1. (a) Explain why $\frac{\text{कम}}{\text{कम}}$ rating reduces in a SCR with increase in its junction surface area. Suggest an external circuit to protect a SCR against large $\frac{\text{कम}}{\text{कम}}$ 2
- (b) What are the advantages of using SCR as a switch over BJT as a switch ? 2
- (c) Suggest and draw a thyristor based full wave ac control circuit to vary light intensity of a bulb. 2
- (d) What is the advantage of dc series and dc shunt motor over each other ? 2
- (e) Under what conditions a synchronous motor will fail to pull into step ? 2

[P.T.O.]

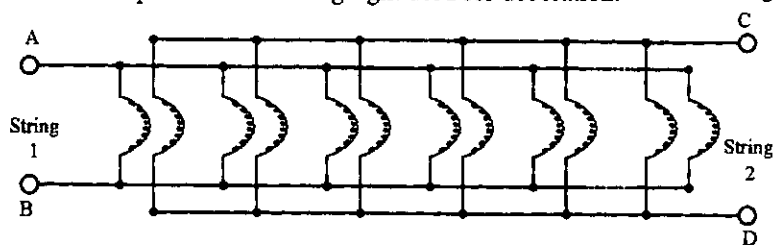2. (a) Using two transistor analogy explain why gate trigger is not required to sustain an SCR in conduction after turning-on. 2
- (b) Discuss various methods to turn-on an SCR 3
- (c) Draw and describe the turn-on characteristics of SCR 2
3. (a) Discuss 2 variations of Bridge Rectifier circuit using 2 diodes and 2 thyristors for R-L load. 3
- (b) Explain how these circuits can be used to control speed of a dc motor. 3
- (c) Which of the two variations is better for inductive load and why? 1
4. (a) Why Commutation Circuits are required in dc power control using SCRs ? 1
- (b) Two strings of parallel connected bulbs, arranged as shown below, are required to be turned on alternately to give an impression of running light used for decoration. 6



Assuming R_1 and R_2 represents the collective load resistance of two strings respectively, suggest a SCR based dc commutation circuit to control the switching of 2 strings of bulbs. Explain operation using required waveforms.

5. (a) Explain voltage commutation in a bridge inverter. 2
- (b) What are the main limitations of a basic series inverter ? Can all limitations be overcome ? Draw and explain an improved series inverter circuit to overcome possible limitations. 5
6. (a) Draw and explain the torque-slip characteristics of an induction motor at constant frequency. 2
- (b) Show and explain the effect of variation in supply voltage and frequency on torque-slip curve. 2
- (c) Derive the expression for starting torque in an induction motor. 2
- (d) How can the starting torque of a slip-ring induction motor can be improved ? 1
7. (a) Explain how back emf makes a dc motor self regulating. 2
- (b) Derive the expression for maximum power developed in a dc motor. 2
- (c) Compare a synchronous and an induction motor. 3