

This question paper contains 4 printed pages.]

Your Roll No. ....

1411

A

**B.Sc. (Hons.)/III**

**ELECTRONICS—Paper 3.6 (XX)**

**(Electrical Technology and Electrical Machines)**

Time : 3 Hours

Maximum Marks : 38

*(Write your Roll No. on the top immediately  
on receipt of this question paper.)*

*Attempt five questions in all, including*

*Question No. 1 which is compulsory. Use of  
non-programmable scientific calculator is allowed.*

1. (a) Define Insulation Resistance. What is its temperature coefficient ?  
2
- (b) The inductance of a coil carrying a current of 2A is 0.5 henry.  
Find the energy stored in it. 2
- (c) Three similar resistors are connected in star across 400-V, 3 phase  
lines. The line current is 5A. Calculate the value of each resistor.  
2
- (d) What are the advantages of polyphase system over a single  
phase system ? 2
- (e) Derive the expression for back e.m.f. for a dc motor. 2
2. (a) Two coils connected in series have resistances of 600  $\Omega$  and 300  
 $\Omega$  at 20°C with temperature coefficient of 0.1% and 0.4%


[P.T.O.]

respectively. Find the resistance of the combination at a temp. of  $50^{\circ}\text{C}$ . What is the effective temperature coeff. of combination?

3

- (b) A cast steel d.c. electromagnet shown. In fig. has a coil of 1000 turns on its central limb. Determine the current that the coil should carry to produce a flux of  $2.5\text{ m}\phi\text{b}$  in the air gap. Neglect leakage. Dimensions are given in cm. The magnetisation curve for cast steel is as under.

FLUX DENSITY	0.2	0.5	0.7	1.0	1.2
( $\phi\text{b}/\text{m}^2$ )					
Amp.-runs/meter	300	540	650	900	1150

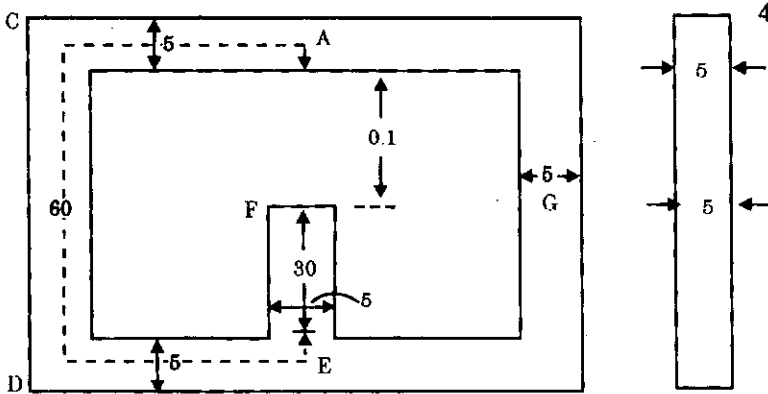

3. (a) A square cross-sectional magnet of side of 4 cm has a strength of  $0.5\text{ m}\phi\text{b}$ . Determine the magnetic flux density. 2
- (b) Explain the concept of mutual inductance. Define coefficient of coupling and derive the expression between self inductances of

two coils, mutual inductance between them and the coefficient of coupling. 5

4. (a) A star connected 3-phase load has a resistance of  $6\Omega$  and an inductive reactance of  $8\Omega$  in each branch. A line to line voltage of 220V is impressed through a 3- $\phi$  auto-transformer. Find the voltage across each branch, line voltages and line currents and total active power. 4
- (b) Deduce the relationship between the phase and line voltages and currents in a three phase star connected circuit. Draw phaser diagram to establish it. 3
5. (a) Calculate the r.m.s. value, the form factor and peak factor of a periodic voltage having the following values for equal time intervals changing suddenly from one value to the next : 0, 5, 10, 20, 50, 60, 50, 20, 10, 5, 0, -5, -10V, -20V, etc. What would be the r.m.s. value of sine wave having the same peak value ? 5
- (b) Write the exponential and polar form of a vector  $5 + j7$ , Illustrate it by means of vector diagram. 2
6. (a) With the help of phaser diagram, explain the operation of a single phase transformer under no load and full load condition. 5
- (b) A sinusoidal flux 0.02 wb (max.) links with 55 turns of a transformer secondary coil. Calculate the r.m.s. value of the induced e.m.f. in the secondary. The supply frequency is 50 Hz. 2
7. (a) A dc generator has the following data :
- (a) no. of poles = 6

- (b) no. of slots = 54
- (c) conductor per slot = 16
- (d) speed of the machine = 100 r.p.m.
- (e) useful flux/pole =  $0.65 \times 10^{-2} \text{ wb}$ .
- (f) Type of winding = wave

Calculate the magnitude of the generated voltage. 2

- (b) How will you find the critical resistance from open circuit characteristics (O. C. C.) of a dc shunt generator, and what is its significance ? 3
- (c) A three phase 11 KV, 50 Hz synchronous generator runs at 1500 r.p.m. Determine the number of poles. 2