

This question paper contains 4 printed pages]

Your Roll No.....

1208

B.Sc. (Hons.) Physics/II Sem. A

Paper-- PHHT-206

DIGITAL ELECTRONICS

Time : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt five questions in all, including

Q. No. 1 which is compulsory.

1. Attempt any ten parts :

- (a) What are the active and passive components ? Give one example of each.
- (b) How are ICs classified on the basis of number of components ?
- (c) What is the meaning of virtual ground in an operational amplifier ?
- (d) Give the pin-out diagram of IC 741.
- (e) Draw the circuit diagram of XOR gate used as an odd-parity generator.

P.T.O.

- (f) How will you obtain an OR gate using only NAND gates ?
- (g) Convert $(175.25)_{10}$ into binary number.
- (h) Add the numbers -8 and -4 .
- (i) Define ROM, PROM and EPROM.
- (j) How many control lines are required to design 8 to 1 multiplexer ?
- (k) Define accuracy and resolution of a digital to analog converter.
- (l) Give any *two* applications of IC 555.
- (m) Give the truth table of a full adder.
- (n) Why D-type flip-flop is called a transparent latch ? $1\frac{1}{2} \times 10^{-15}$
2. (a) Draw the block diagram of a CRO and label all its parts.
Explain how a CRO can be used to measure : 10
- (i) Current and
- (ii) Phase difference.
- (b) What do you mean by an integrated circuit ? Mention the various steps involved in the fabrication of ICs.

3. (a) Derive an expression for the gain of an operational amplifier in an inverting mode. 3
- (b) Describe how an op-amp can be used to perform the mathematical operation of an integrator. If the input is given by $V_{in} = V_o \sin \omega t$, what is the expression for its output ? Also, draw the input and output waveforms. 7
- (c) Draw the logic circuit for a 4-input multiplexer and explain its functioning. 5
4. (a) Draw a circuit diagram of an astable multivibrator using IC 555 and obtain an expression for its frequency. Obtain the condition to produce square wave. 5
- (b) Explain the working of a R-2R ladder network based on D/A converter. How many steps are there in the output of an 8-bit D/A converter ? What are the advantages of a R-2R ladder over binary weighed resistor ? 5
- (c) Draw the 4-bit shift register in serial-in serial-out configuration and the time diagram for the 1011 input. 5

5. (a) Give the truth table of JK flip-flop having preset and Clear conditions. How is racing condition eliminated in JK flip-flop ? Give the circuit diagram and explain its functioning. 4
- (b) Draw a circuit for a decade counter and explain its functioning. 6
- (c) Minimize the following logic expression using K-map and realize it with NAND gates : 5
- $$F(A, B, C, D) = \Sigma(0, 1, 2, 5, 7, 8, 9, 10, 13, 15).$$
6. (a) (i) Give an equivalent circuit of an operational amplifier. 5
- (ii) Give the characteristics of an ideal operational amplifier. 5
- (b) Draw the circuit diagram of 3 to 8 decoder and explain its functioning. 5
- (c) Explain with an appropriate logic circuit diagram the working of a 4-bit adder/subtractor. 5
7. (a) Discuss the application of summing amplifier as : 5
- (i) an adder and
- (ii) a subtractor.
- (b) Draw the circuit diagram of a RS flip-flop and explain its working. 6
- (c) Explain the working of a simple decimal to BCD encoder. 4