

This question paper contains 2 printed pages.

1210-A

Your Roll No.

B.Sc. (Hons.) PHYSICS / II Sem.

A

Paper— PPHP – 206
(Digital Electronics)

Time : 1 hour

Maximum Marks : 20

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt any twenty questions. Each question carries 1 mark.

1. Which of the following are analog quantities :

- (a) Ten-position switch (b) Altitude of an aircraft
(c) Pressure in a car tyre (d) Timer setting on a washing machine

2. Define (a) a bit, and (b) a byte.

3. What do '74' and '00' in 74LS00 stand for ?

4. Draw the circuit of a two-input AND gate using NAND gates only.

5. Find the truth table for the following Boolean expression

$$Y = A(\overline{B + C}) + B$$

6. Simplify the following Boolean expression using Boolean algebra.

$$Y = (A + B)(\overline{A} + B)$$

7. Draw the K-map for the following boolean equation

$$Y = \overline{A}\overline{B} + AB + AC + ABC$$

and simplify it.

8. What is the difference between a Half Adder and a Full Adder?

9. Make the truth table of a Full Subtractor and write down the Boolean expressions for DIFFERENCE and BORROW.

10. Draw the circuit of a RS flip-flop using NAND gates.

11. Why is a D flip-flop called a transparent latch ?

P.T.O.

12. What is a *race – around* condition in a *JK flip – flop* ? Name any method to overcome this condition.
13. What are the two main functions of a shift-register ?
14. Why are synchronous counters faster than asynchronous counters ?
15. Using *JK/D flip – flops* design a divide-by-6 ripple counter.
16. What is an *Encoder*?
17. In a *seven – segment LED* Display, which segments will glow to display the symbol 6 ?
18. Define the resolution of a *D/A* converter.
19. How many bits are required for a *DAC* for a resolution of 20 *mV* if the full scale output voltage is 10 *V* ?
20. Give four characteristics of an ideal Op-Amp ?
21. What is the meaning of virtual ground in an Op-Amp ?
22. Draw the circuit of an inverting amplifier of gain 10 using an Op-Amp.
23. An Op-Amp has a gain-bandwidth product of 15 *MHz*. Determine the bandwidth of the Op-Amp when $A_{CL} = 500$.
24. What is the duty cycle of an astable 555 timer ?
25. Determine the frequency of a 555 oscillator for $R_A = R_B = 2.2 \text{ k}\Omega$, and $C = 2000 \text{ pF}$.