

This question paper contains 4 printed pages]

Roll No.

--	--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 1466

Unique Paper Code : 2221302

F-7

Name of the Paper : Digital System and Applications

Name of the Course : B.Sc. (Hons.) Physics/(II)/Admitted previously under FYUP

Semester : III

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt Five questions in all.

Question No. 1 is compulsory.

1. Answer any five of the following :

5×3

(a) Using Boolean Algebra prove that :

$$\bar{A}B + BC + AC = \bar{A}B + AC.$$

(b) What is an integrated chip ? Give two advantages and disadvantages of an IC.


(c) Add the decimal numbers 48 and 27 after converting each to its BCD code. Represent the answer in the BCD code.

(d) What is the function of the Reset and Hold signals in 8085 microprocessor.



(e) Implement 4 input NAND gates using 2-input NAND gates.

P.T.O.

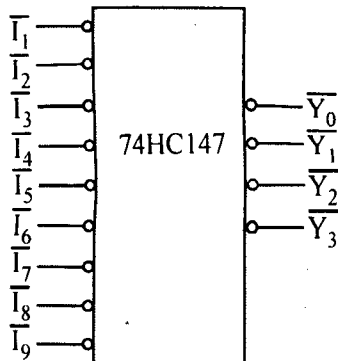- (f) Realize $F(ABC) = \sum m(0, 1, 3, 4, 8)$ using an 8 to 1 multiplexer. Use only the block diagram of the multiplexer.
- (g) A binary counter is being pulsed by a 256 KHz clock signal. The output frequency from the last flip-flop is 500 Hz. Determine the number of flip-flops used in the counter and the MOD number.
- (h) Draw the truth-table of a full subtractor.
2. (a) Simplify the expression using Karnaugh-map and draw its logic circuit using NAND gates only :
- $$f = \sum m(4, 6, 9, 10, 11, 14, 15) + \sum d(0, 1, 2, 3). \quad 6$$
- (b) What is PROM and E-PROM ? Describe the construction and working of a 8×4 diode ROM to write nibbles from 0000 to 0111. 6
- (c) Subtract $(-35)_{10}$ from $(-15)_{10}$ using 2's complement method. 3
3. (a) Draw a circuit of parallel in-serial out shift register and explain its working. 8
- (b) Differentiate between demultiplexer and decoder. 4
- (c) In the figure below, 74HC147 is a decimal to BCD encoder. What sort of input conditions would be required to generate the code for the number 7 and how that numerical quantity would be represented on the output (Y) lines ? 3



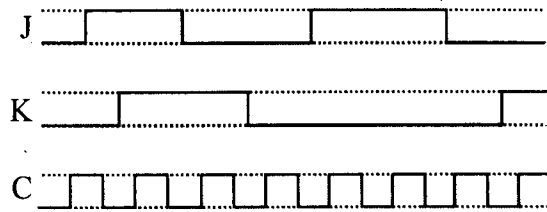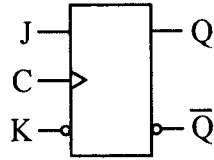4. (a) Determine the Q output of the J-K flip-flop, if initially the flip-flop is reset. 4



- (b) Draw the circuit diagram and explain the working of a 4-bit adder-subtractor. 6

- (c) Give the truth-table and the circuit diagram of a JK flip-flop having preset and clear conditions. How is racing condition eliminated in JK flip-flop ? 5

5. (a) What are ring counters and where is it used ? 3

- (b) Explain the working of a decade counter with the help of its circuit diagram. Draw its output waveforms and also write its truth-table. 8

- (c) Explain glitches. How do we remove them from the output ? 4

6. (a) Explain the function of pins 2 and 4 of the IC 555. 3

- (b) Draw the circuit diagram of 555 timer as a monostable multivibrator and explain its working. 6

- (c) Design a monostable multivibrator using 555 timer to get an output with a positive pulse of 10 ms. For this multivibrator, draw the output waveform a pin 3 when the input trigger has pulse width 2 ms and time periods are :
- (i) 15 ms
- (ii) 9 ms. 6
7. (a) Give the timing diagram of the following : 6
- | Memory Address | Machine Code | Mnemonics |
|----------------|--------------|-----------|
| 2050H | 41H | MOV B, C |
- (b) Describe with an example, each of 1 byte, 2 byte and 3 byte instruction in 8085 microprocessor instruction set. 6
- (c) The memory requirement for an 8085A microprocessor based system is 24K-bytes RAM chips and 8K-bytes ROM chips. If memory chips of size $1K \times 4$ bits are available for both RAM and ROM, how many RAM and ROM chips are required ? 3
8. (a) Write an assembly language program to subtract 5DH from FCH stored in memory locations 2006H and 2007H respectively using (i) direct and (ii) indirect addressing modes. The difference is to be stored in memory location 2008H and borrow in 2009H. 5
- (b) Distinguish between memory-mapped I/O and peripheral-mapped I/O. 3
- (c) What are flags ? If the accumulator contain 0BH and register C contain 05H, which flags are affected when CMP C is executed ? 4
- (d) Define instruction cycle, machine cycle and T-states. 3