

[This question paper contains 2 printed pages.]

Sr. No. of Question Paper : 2145 **GC-3** **Your Roll No.....**

Unique Paper Code : 32223904

Name of the Paper : Basic Instrumentation Skills

Name of the Course : B.Sc. (Hons.) Physics (CBCS) Skill Enhancement Course

Semester : III

Duration : 3 Hours

Maximum Marks : 50

Instructions for Candidates

1. Write your Roll No. on the top immediately on the receipt of this question paper.
2. Attempt any **five** questions in all.

1. (a) Explain accuracy, precision and resolution of an instrument.
(b) A set of independent voltage measurement taken by four observers was recorded as 117.02 V, 117.11 V, 117.08 V and 117.03 V. Calculate average voltage and average deviation. (5,5)
2. (a) How is an electronic voltmeter better than a conventional VOM ? Explain it in terms of input impedance and sensitivity.
(b) Discuss the loading effect of a multimeter with the help of an example.
(c) Calculate the value of multiple resistance on the 50 V range of a dc voltmeter that uses a 500 μ A meter movement with an internal resistance of 1 k Ω . (4,4,2)
3. (a) Explain the principle of working of DSO.
(b) How is the electrostatic focusing achieved in CRT ? Explain it with the help of a diagram. (5,5)

P.T.O.

4. (a) What is a wave analyzer ? Explain it with the help of a diagram.
- (b) Explain the working of a pulse generator with the help of a block diagram. (5,5)
5. (a) What are the advantages of using digital instruments over analog instruments ?
- (b) Draw the basic circuit diagram for a Q-meter. Explain its operation and write the equation for Q factor. (3,7)
6. (a) Discuss any LCR bridge in detail with the help of a diagram.
- (b) A Maxwell Bridge is used to measure inductive impedance. At balance, the bridge constants are $C_1 = 0.01 \mu\text{F}$, $R_1 = 470 \text{ k}\Omega$, $R_2 = 5.1 \text{ k}\Omega$, $R_3 = 100 \text{ k}\Omega$. Find the series equivalent of unknown impedance. (6,4)
7. (a) How is the universal counter used for the measurement of frequency ?
- (b) What is a multimeter ? How is it used as a voltmeter ? (5,5)