

[This question paper contains 4 printed pages.]

Sr. No. of Question Paper : 2389

F-4

Your Roll No.....

Unique Paper Code : 2221403

Name of the Course : B.Sc. (Hons) Physics

Name of the Paper : Analog System and Applications

Semester : IV

Duration : 3 Hours

Maximum Marks : 75

**Instructions for Candidates**

1. Write your Roll No. on the top immediately on receipt of this question paper.
2. Attempt five questions in all.
3. Question No. 1 is compulsory.
4. Non programmable calculators are allowed.


1. Attempt any five of the following

- (a) Draw the output-characteristics of a solar cell and label important parameters.
- (b) Define accuracy and resolution for an D/A converter
- (c) What is the difference between differential and common mode inputs for an op-amp.
- (d) The energy gap of the semiconducting material of an LED is 1.37eV. What is the wavelength of the emitted light?
- (e) Show that  $I_c = \beta I_B + (1 + \beta) I_{CBO}$
- (f) Distinguish between Class A and Class B amplifiers with the help of load line and Q point.
- (g) Define PIV, ripple factor and rectification efficiency of a rectifier.

(3×5=15)

P.T.O.

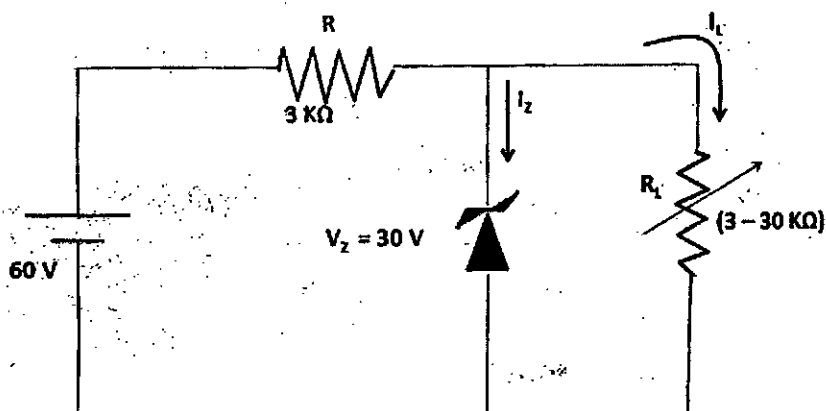2. (a) Obtain an expression for the barrier width of a p-n junction diode, assuming a step junction.
- (b) In a Ge sample a donor type impurity is added to the extent of 1 atom per  $10^8$  Ge atoms. Find the concentration of electrons and holes in the sample. Given  $N_i = 2.5 \times 10^{13}$  electrons /  $\text{cm}^3$  and number of Ge atoms is  $4.41 \times 10^{22}$  per  $\text{cm}^3$ . (12,3)
3. (a) Explain the working of a center-tap full wave rectifier using suitable diagrams and obtain the expressions for
- ripple factor and
  - rectification efficiency.
- (b) Find the current through the zener diode in the following circuit when load resistance  $R_L$  is :
- $30\text{k}\Omega$ ,
  - $5\text{k}\Omega$
  - $3\text{k}\Omega$



(11,4)

4. (a) Describe "load line" and "Q-point" of a transistor in CE configuration with appropriate diagram.
- (b) Draw a diagram for the voltage divider bias circuit of an n-p-n transistor in CE configuration. Derive an expression for the stability factor (S) using Thevenin's equivalent circuit.
- (c) Find the Q - point of the fixed bias circuit with  $R_C = 4k\Omega$ ,  $R_B = 1.2 M\Omega$ ,  $V_{CC} = 9.0 V$ ,  $V_{BE} = 0.2 V$  and  $\beta = 80$ . (4,4,7)
5. (a) Using 'h' parameters, obtain expressions for current gain, voltage gain, input impedance and output impedance for transistor in CE configuration.
- (b) For a 4-bit binary R-2R ladder D/A converter the input levels are 0=0V and 1=+10V. Find the output voltage caused by
- (i) 0011,
- (ii) 1001 and
- (iii) 1111. (12,3)
6. (a) Describe the conditions for sustained oscillations in an oscillator? Derive an expression for the frequency of a Colpitt's oscillator.
- (b) A phase shift oscillator has three identical RC sections  $R_L=R=10k\Omega$  and  $C=0.01\mu F$ . Determine the frequency of oscillation.— (12,3)
7. (a) Explain with the help of an appropriate circuit diagram the working of a logarithmic amplifier using an op-amp.
- (b) What would be the output of an op-amp in the inverting mode if input resistance is 1 k $\Omega$  and feedback resistance is
- (i) 2 k $\Omega$  and

- (ii)  $20\text{k}\Omega$  for a dc input signal of  $1.5\text{ V}$ ? ( $V_{\text{sat}} = \pm 14\text{ V}$ ).
- (c) Draw the circuit of an Op-amp as an integrator and find an expression for its output. Draw the output waveform when the input to the integrator is a square wave. (6,3,6)