

This question paper contains 7 printed pages.]

Your Roll No.

1231

B.Sc. (Hons.) / III A

PHYSICS – PAPER – XXI

(Electronic Devices : Physics and Applications)

Time : 3 Hours

Maximum Marks : 38

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt five questions in all.

Question No. 1 is compulsory.


Attempt one question from each Section.

Use of calculator (non-scientific) is allowed.

1. Attempt any four parts : $4 \times 1 \frac{1}{2}$

- (a) Discuss any two advantages and one disadvantages of FM over AM.

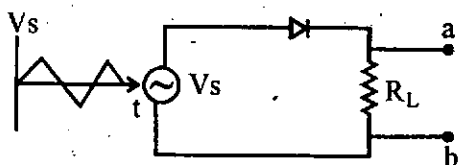
- (b) A light emitting diode (LED) formed from an alloy semiconductor has $E_g = 1.9 \text{ eV}$. Find the wavelength of the emitted light when the diode is forward biased. ($h = 6.63 \times 10^{-34} \text{ J-sec}$)
- (c) Draw the waveform that will be shown in a CRO across a - b



- (d) What is Noise ? Mention any two sources of Noise in a transistor.
- (e) How does the junction capacitance of reversed biased p-n diode varies with applied voltage ?
- (f) Draw the h-parameter equivalent circuit for a transistor in CE mode.

SECTION - A

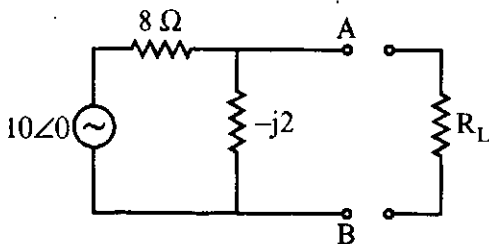2. (a) State and prove Maximum power transfer theorem. 5
- (b) Find the Thevenin equivalent circuit for the given network between A and B. 3



3. (a) For an unbiased p-n junction diode, sketch the variation of space charge, electric field and potential as a function of distance across the junction. Obtain the expression for potential barrier and widths of depletion layer. 5
- (b) The reverse saturation current of a p-n junction diode is $5\ \mu\text{A}$ at 300 K. Find the voltage to be applied to obtain a forward current of $50\ \mu\text{A}$. ($k_B = 1.38 \times 10^{-23}\ \text{J/K}$). 3

SECTION - B


4. (a) Explain working of a diode detector circuit and sketch the output waveform. Obtain a relation between time constant RC of the circuit and modulating frequency. 6
- (b) A carrier wave of 100 watts is subjected to 50% amplitude modulation. Determine
- (i) power of the modulated wave.
- (ii) power contained in each of the side bands. 2
5. (a) Obtain the expression for total collector current flowing through CE configuration of a transistor taking into account leakage current. 2
- (b) With the help of a necessary circuit diagram, draw and discuss the drain (static) characteristics of an n-channel FET. 3
- (c) Explain how is a zener diode used in voltage regulation under both varying input and varying load conditions. 3

SECTION - C

6. (a) Draw the circuit diagram of a two-stage R-C Coupled Amplifier. Draw the a.c. equivalent circuit at mid, low and high frequency. Calculate the voltage gain in the mid frequency region. 5
- (b) An Amplifier has a voltage gain of 100. The feedback ratio is 0.04. Calculate 3
- (i) the voltage gain with feedback.
- (ii) the output voltage of the feedback amplifier for an input voltage 40 mV.
- (iii) the feedback factor.
7. (a) Explain the need of biasing and stabilization in an amplifier. Draw and discuss the voltage divider bias circuit. Derive an expression for its stability factor. 5

- (b) Draw the load line for the following circuit, also locate the Q-point ($\beta = 100$).

3

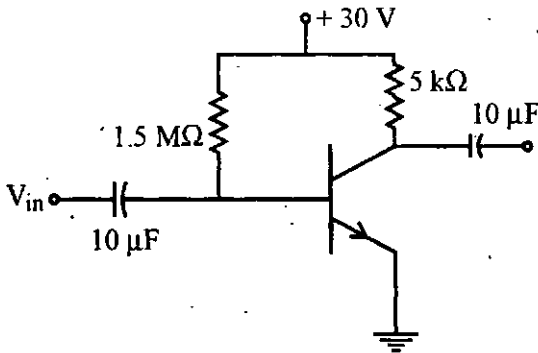

SECTION - D

8. (a) Explain the operation of a Colpitt's oscillator with the help of a circuit diagram. Derive an expression for the frequency of oscillation and condition for sustained oscillation.

6

- (b) A piezoelectric crystal used in a crystal oscillator is resonant at 450 kHz. For this frequency, its equivalent inductance and series resistance are 3.5 H and 9050 Ohm respectively. What is the Q value of the crystal?

2

9. (a) What is a relaxation oscillator ? Draw and discuss the working of a UJT sweep generator and calculate the time period of oscillator. 6

(b) Draw the labelled circuit diagram of an astable multivibrator using BJT. 2
