

This question paper contains 4 printed pages]

Roll No.

--	--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : **6218**

Unique Paper Code : **222504**

D

Name of the Paper : **Electronic Devices (PHHT-518)**

Name of the Course : **B.Sc. (Hons.) Physics**

Semester : **V**

Duration : **3 Hours**

Maximum Marks : **75**

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt *five* questions in all. *All* questions carry equal marks.

Question No. **1** is compulsory. Use of Scientific Calculator is allowed.

All symbols have their usual meaning.

$$(h = 6.63 \times 10^{-34} \text{ Js}, k_B = 1.38 \times 10^{-23} \text{ J/K}, q = 1.6 \times 10^{-19} \text{ C}, c = 3 \times 10^8 \text{ m/s.})$$

1. Answer the following questions (any *five*) :

5×3=15

(a) Calculate I_C and I_E for a transistor that has $\alpha = 0.98$ and $I_B = 100 \mu\text{A}$.


(b) The wavelength of light emitted by a certain LED is 60 nm. Find the energy gap in eV.

(c) Determine peak point emitter voltage for a UJT transistor if $V_{BB} = 20 \text{ V}$ and $\eta = 0.6$.

P.T.O.


- (d) What is the position of the Fermi level in an intrinsic semiconductor ? How does its position change when :
- (i) donors and
 - (ii) acceptors
- are added to the semiconductor ?
- (e) Show that negative feedback helps in reduction of noise in amplifiers.
- (f) Give a short note on photodiode.
- (g) Differentiate between amplifier and oscillator. State Barkhausen Criterion for self-sustained oscillations.
2. (a) Explain the concept of potential energy barrier.
- (b) Derive the Volt-Ampere (V-I) equation for a $p-n$ junction diode.
- (c) For an abrupt Ge $p-n$ junction doped with donor and acceptor concentrations of $N_d = 10^{23} \text{ m}^{-3}$ and $N_a = 10^{22} \text{ m}^{-3}$, calculate the potential barrier if intrinsic carrier density $n_i = 10^{13} \text{ cm}^{-3}$. Assume $KT/q = 0.026 \text{ V}$. 2,10,3
3. (a) Draw circuit diagram of a Full Wave rectifier. Calculate I_{dc} , I_{rms} , ripple factor, efficiency of rectification.
- (b) With the help of energy band diagram, explain current V_s . voltage characteristics of a Tunnel diode in forward and reverse biasing conditions. 8,7
4. (a) Why the voltage divider bias circuit is preferred to Fixed bias circuit for a BJT ? Calculate stability factors S of voltage divider bias circuit.

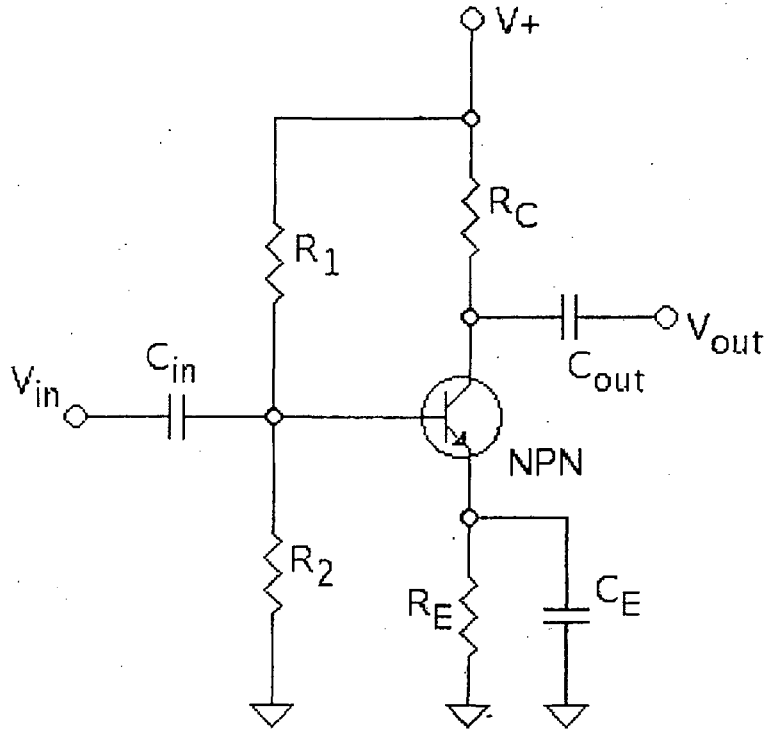- (b) Determine the dc bias voltage and the current I_c for the voltage-divider configuration if $V = 22 \text{ V}$, $R_1 = 39 \text{ k}\Omega$, $R_2 = 3.9 \text{ k}\Omega$, $R_c = 10 \text{ k}\Omega$, $R_E = 1.5 \text{ k}\Omega$, $C_{in} = C_{out} = 10 \mu\text{F}$, $C_E = 50 \mu\text{F}$ and $\beta = 140$. 8,7



5. (a) Draw the circuit diagram of RC coupled amplifier. Give its ac equivalent circuit in different frequency ranges. Derive its voltage gain in low frequency region.
- (b) Calculate hybrid parameters of a CE single stage transistor amplifier :
- (i) with a.c. output shorted having $I_b = 20 \mu\text{A}$, $I_c = 1 \text{ mA}$, $V_{be} = 22 \text{ mV}$ and $V_{ce} = 0 \text{ V}$
- (ii) with a.c. input open circuited having $I_b = 0 \mu\text{A}$, $I_c = 30 \mu\text{A}$, $V_{be} = 0.25 \text{ mV}$ and $V_{ce} = 1 \text{ V}$. 8,7

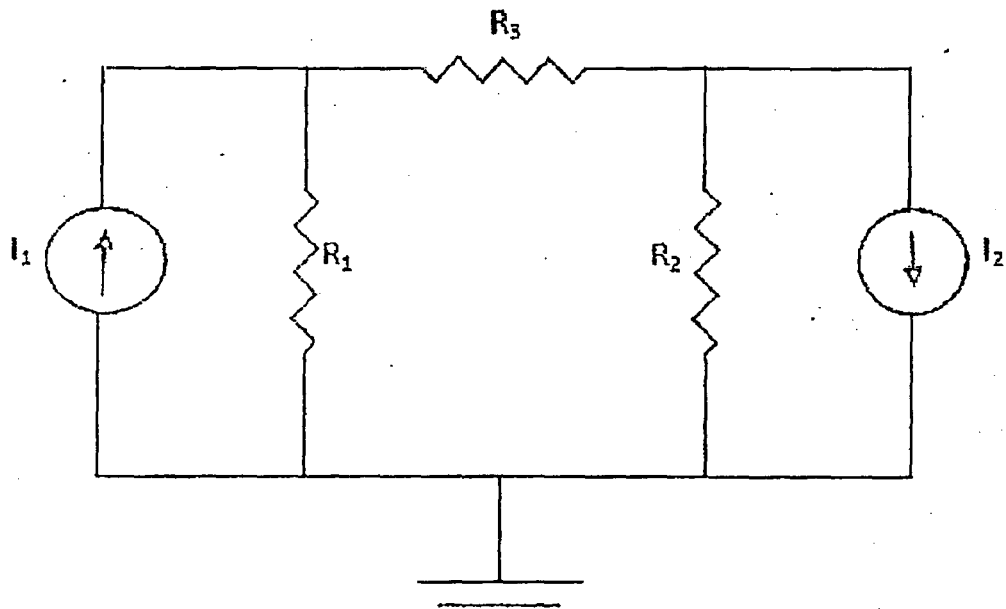- 6. (a) Explain the working of a transistor astable multivibrator. Obtain an expression for time period and draw the output waveform for both the transistors.
- (b) Explain the working of a JFET. Draw and discuss the transfer and drain characteristics of an n -channel JFET. Also give its equivalent circuit. 7,8
- 7. (a) What is amplitude modulation ? Show that the amplitude modulated wave consists of carrier and two side bands.
- (b) Determine the nodal voltages for the given network if $I_1 = 4 \text{ A}$, $I_2 = 2 \text{ A}$, $R_1 = 2 \Omega$, $R_2 = 6 \Omega$, $R_3 = 12 \Omega$.



- (c) Convert the following π to T network. 8,5,2

