

This question paper contains 3 printed pages]

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 855

Unique Paper Code : 222504

G

Name of the Paper : Electronic Devices (PHHT 518)

Name of the Course : B.Sc. (Hons.) Physics

Semester : V

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Question No. 1 is compulsory.

Attempt Five questions in all.

1. Answer the following questions (any five) :

(a) What is the position of the Fermi level in an intrinsic semiconductor ? How does its position change when :

(i) donors and

(ii) acceptors

are added to the semiconductor ?

3

(b) Give two differences between BJT and FET.

3


(c) A phase shift oscillator has three identical RC sections $R_L = R = 10 \text{ k}\Omega$ and $C = 0.01 \text{ }\mu\text{F}$. Determine the frequency of oscillation.

3

P.T.O.

- (d) Convert the following π to T network :

3

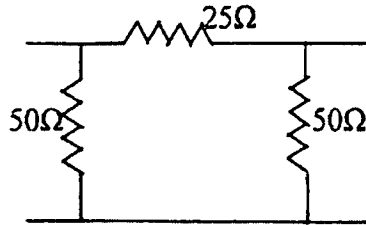


- (e) Compare CE, CB and CC amplifiers in terms of current gain and voltage gain. 3

- (f) For an abrupt $p-n$ junction in Ge doped with donor and acceptor concentrations of $N_d = 10^{23} \text{ m}^{-3}$ and $N_a = 10^{22} \text{ m}^{-3}$. Calculate the height of the potential barrier. 3

2. (a) Find voltage across R using mesh analysis.

7

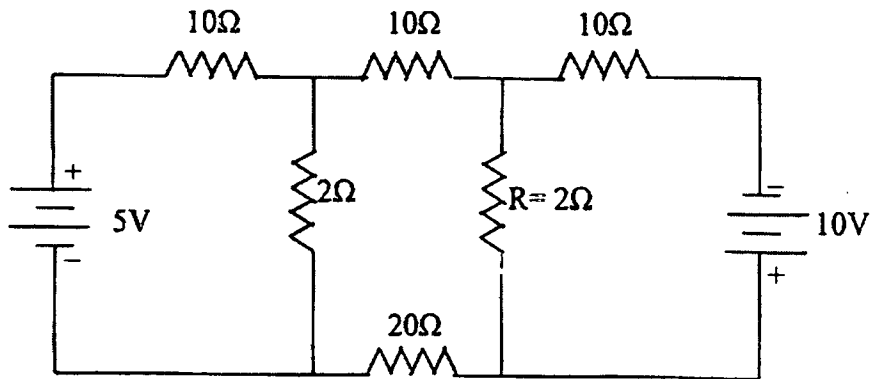

- (b) For an unbiased $p-n$ junction, sketch the variation of the space charge, electric field and electric potential as a function of distance across the junction giving the relevant equations. 8

3. (a) For a four terminal network derive its T equivalent circuit in terms of short circuit and open circuit impedances. 7

- (b) Explain the formation of depletion layer in a $p-n$ junction diode. Derive the expressions for potential barrier and width of depletion layer for a $p-n$ step junction diode. 8

4. (a) With the help of energy band diagram, explain current I vs. voltage characteristics of Tunnel diode in forward and reverse biasing conditions. 8
- (b) Give advantages of LED over a conventional light bulb. 4
- (c) The wavelength of light emitted by a certain LED is 60 nm. Find the energy gap in eV. 3
5. (a) What is negative feedback ? How does it affect the input and output impedance of an amplifier (support your answer with derivation) ? 8
- (b) A transistor used in CE configuration has the following set of h -parameters : $h_{ie} = 1 \text{ k}\Omega$, $h_{fe} = 100$, $h_{re} = 5 \times 10^{-4}$ and $h_{oe} = 2 \times 10^{-5} \text{ S}$ with $R_s = 2 \text{ k}\Omega$ and $R_c = 5 \text{ k}\Omega$, determine input impedance, voltage gain, output impedance and current gain. 7
6. Draw the circuit diagram of a RC coupled amplifier. Draw the a.c. equivalent circuit at mid, low and high frequency respectively. Calculate the voltage gain in mid and low frequency regions. 15
7. (a) Explain the basic concept of amplitude, frequency, and phase modulation. Define modulation index and derive power relations between carrier wave and side bands in an Amplitude Modulated wave. 10
- (b) Draw the circuit diagram of a diode detector for demodulation of AM wave and explain its working. 5