

This question paper contains 4 printed pages]

Your Roll No.

197

B.Sc. (Gen.)/II

QUALIFYING : DIGITAL ELECTRONICS—Paper IV

Time : 3 Hours

Maximum Marks : 100

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt *five* questions in all,

Question No. 1 is compulsory.

All questions carry equal marks.

1. Attempt any *five* questions : 5×4=20

(a) Do the following conversions :

(i) $(634)_8$ to binary

(ii) (0.640625) to its octal equivalent.

(iii) Graycode (101011) to its binary equivalent.

P.T.O.

- (b) Design XNOR gate using NOR gate.
- (c) Simplify the following using De Morgan's theorem
 $[((AB)'C)''D]'$.
- (d) Design full subtractor using half subtractor.
- (e) Define :
- (i) Power dissipation
- (ii) Propagation delay
- (iii) Noise margin.
- (f) Define race around condition.

2. (a) Reduce the expression : $6\frac{2}{3}$

$$f = A \left[B + \bar{C} \left(\overline{AB + AC} \right) \right].$$

- (b) Design a half subtractor in SOP showing K-map for
 difference and borrow. $6\frac{2}{3}$
- (c) Find the complement of : $6\frac{2}{3}$

$$AB + \overline{AC} + A\bar{B}C.$$

3. (a) Design an OR gate (two input) using diodes and resistance. Explain the working using truth table. $6\frac{2}{3}$
- (b) Write advantages of I²L families over other families. $6\frac{2}{3}$
- (c) Design NAND gate using NMOS logic family. $6\frac{2}{3}$
4. (a) Design a monostable multivibrator with $T_{HIGH} = 1.1 \text{ ms}$. $6\frac{2}{3}$
- (b) Draw the circuit of RS flip-flop and explain its working using truth table. $6\frac{2}{3}$
- (c) Design a MOD-8 counter. $6\frac{2}{3}$
5. (a) Design a 3-bit weighted DAC circuit. (Digital to analog converter circuit). Also explain its working. 11
- (b) What are the output voltages caused by each bit in a 5-bit ladder if the input levels are $0 = 0V$ and $1 = 10V$. 9
6. Write short notes on any two : $10 \times 2 = 20$
- (a) Up-Down counter.
- (b) ROM
- (c) D' Morgan's theorem.

7. (a) Write a program in assembly language to add two hex numbers by direct addressing mode. 10
- (b) Specify the addressing modes of the following instructions : 3.3×3
- (i) STA 2050
- (ii) ADI 50H
- (iii) STAX D.