

This question paper contains 4+2 printed pages]

Your Roll No.

238

B.Sc. Prog./II

C

EL-201 - ANALOG AND DIGITAL CIRCUITS

(NC –Admissions of 2005 and onwards)

Time : 3 Hours

Maximum Marks : 75

(Write your Roll No on the top immediately on receipt of this question paper.)

Attempt *five* questions in all. selecting at least

two questions from each Section 'A' and Section 'B'.

All questions carry equal marks.


Section 'A'

1. (a) State and explain Thevenin's theorem. 5

P.T.O.


- (b) Derive the condition for transfer of maximum power from a source to a load. 5

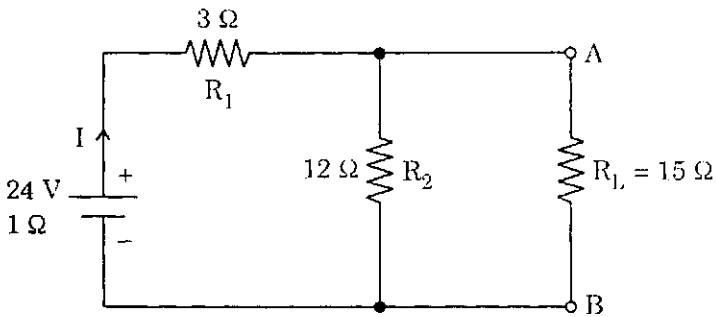- (c) Apply Thevenin's theorem to the circuit given below and find the current through R_1 . 5



2. (a) Describe the various methods used for transistor biasing. State their advantages and disadvantages. 7
- (b) What do you understand by class A, class B and class C power amplifiers? 3

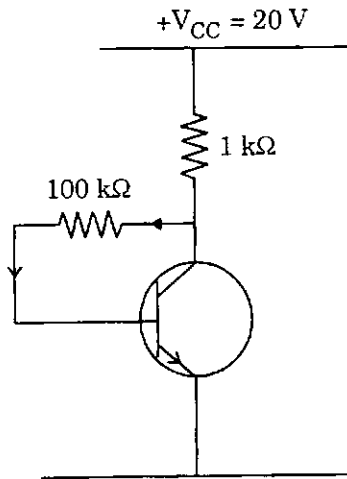- (c) Fig. below shows a silicon transistor biased by feedback resistor method. Determine the operating point. Given $\beta = 100$.



3. (a) With a neat sketch, explain the working of a full-wave bridge rectifier.
- (b) Derive an expression for the efficiency and ripple factor of a full-wave rectifier.

Section 'B'

4. (a) Perform the operation :

$$(A^7B)_{16} - (4^76)_8 - (11011)_2 = ()_{16}. \quad 6$$

- (b) Subtract 38_{10} from 82_{10} using 2's complement method. 5

- (c) Prove the following Boolean expression :

$$\overline{(\overline{A + BC})} \cdot \overline{(\overline{AB} \cdot \overline{C})} = A + B \oplus C. \quad 4$$

5. (a) Find MSP for the Boolean expression :

$$F(A, B, C, D) = \sum m(1, 3, 4, 5, 9, 10, 11) + \sum \phi(6, 8)$$

using Karnaugh method and implement it using only

\AND gates. 9

- (b) Draw and explain the circuit for a TTL logic family

NAND gate. 6

6. (a) Draw the logic circuit diagram of 4-bit adder-cum-subtractor. 5
- (b) Implement a full-adder with two 4×1 MUXs using block diagram. 5
- (c) A combinational circuit is defined by the following Boolean function. Design the circuit with a decoder and external gate :

$$F = \bar{x}\bar{y}\bar{z} + x\bar{z} + \bar{x}y. \quad 5$$

7. (a) Draw the logic circuit diagram of a Master-Slave JK Flip-Flop and explain how it prevents racing ? 8
- (b) Draw the logic circuit diagram of 4-bit serial-in-serial out controlled shift-left register. 7

8. (a) Draw the logic circuit diagram of 4-bit asynchronous UP DOWN counter and explain its operation. 7
- (b) How does a static RAM cell differ from a dynamic RAM cell ? 3
- (c) Draw a block diagram for Bipolar 256×4 ROM and explain its working. 5