

This question paper contains 3 printed pages]

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 6857

Unique Paper Code : 222361

D

Name of the Paper : Electronics Instrumentation (ELPT-303)

Name of the Course : B.Sc. (Physical Science)

Semester : III

Duration : 3 Hours

Maximum Marks : 75

*(Write your Roll No. on the top immediately on receipt of this question paper.)*

Attempt any *Five* questions.

1. (a) Describe the working of d' Arsonval meter movement ? Explain how it can be modified to work as ammeter and hence find a relation between the internal resistance ( $R_m$ ) and shunt resistance ( $R_s$ ). 8
- (b) What values of shunt resistances are required for using a  $50 \mu\text{A}$  meter movement with an internal resistance of  $5 \text{ k}\Omega$  for measuring  $100 \mu\text{A}$  and  $500 \mu\text{A}$  ? 4
- (c) What basic precautions should be taken while using an ammeter ? 3

P.T.O.

2. (a) Discuss the working of ramp type digital voltmeter with the help of block diagram. 8
- (b) Explain the working of a series-type ohmmeter. Deduce the expressions for current-limiting resistor and zero-adjust resistor used. 7
3. (a) Draw the block diagram of a CRO and briefly explain the function of each block. 9
- (b) Explain the following terms :
- (i) Fluorescence .
- (ii) Phosphorescence .
- (iii) Aquadag. 6
4. (a) Discuss the electrostatic focussing system of a CRT. 5
- (b) Show that for a given accelerating voltage  $E_a$  and for particular dimensions of CRT, the deflection of electron beam is directly proportional to the deflecting voltage indicating CRT to be a linear device. Derive the deflection sensitivity of CRT. 10
5. (a) Draw the block diagram of Vertical Deflection System of a CRO and describe the function of each of its components. 12
- (b) What is the need for a trigger circuit in a CRO ? 3

6. (a) Draw the circuit diagram and explain how a square wave is generated using an Astable multivibrator. Also explain the term duty cycle, rise and fall time. 12
- (b) Draw the block diagram of sweep frequency generator. 3
7. Write short notes on any *two* : 7½, 7½
- (i) Transducers and their applications
- (ii) Lissajous patterns and their significance
- (iii) Delay lines
- (iv) Sampling Oscilloscope.