

This question paper contains 4 printed pages]

Roll No. 

--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 62

Unique Paper Code : 222171

G

Name of the Paper : Electronics-I Network Analysis (ELPT-101)

Name of the Course : B.Sc. Physical Science/Applied Physical Science

Semester : I

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt any five questions.

All questions carry equal marks.

1. (a) Find the effective value of the function :

$$y = 50 + 30 \sin \omega t .$$

4

- (b) State and explain Kirchoff's current law in detail.


7

- (c) What are the active and passive elements in the circuit ? Give one example of each.

4


2. (a) Find the current supplied by the 60 V source using the mesh current method.

6

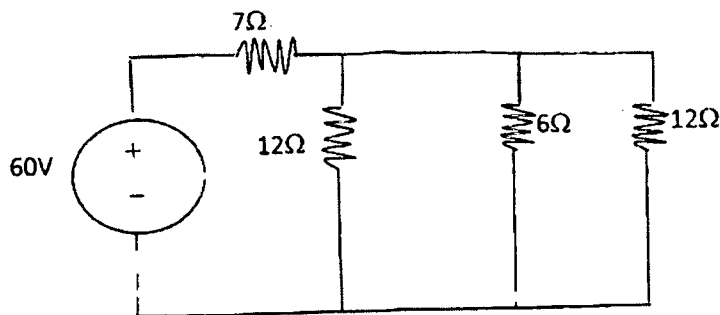


P.T.O.

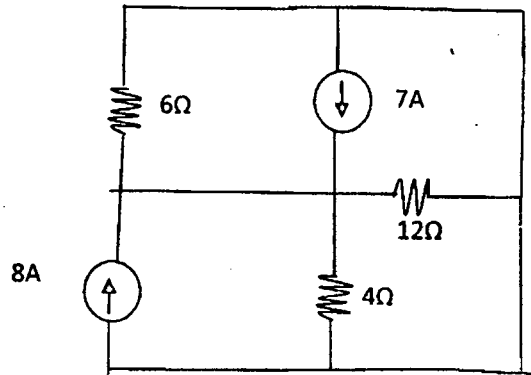- (b) Given  $V_1 = 25.0 \angle 143.13^\circ$  and  $V_2 = 11.2 \angle 26.57^\circ$ , find the ratio  $V_1/V_2$  and the sum  $V_1 + V_2$ . 4
- (c) State and prove Millman's theorem. 5
- 3. (a) For the network below solve for all currents using nodal analysis. What is the power absorbed by 8A element ? 8




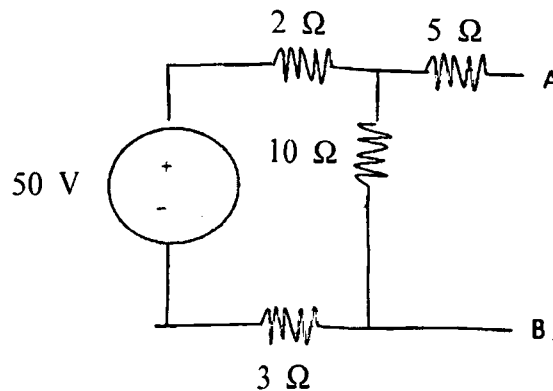- (b) State and explain Thevenin and Norton Theorems. 7
- 4. (a) Find the value of R between AB so that maximum power is transferred by the source. What is the maximum power through the load ? 6




- (b) Using the superposition theorem find  $I_s$  in the circuit shown in figure below :

9

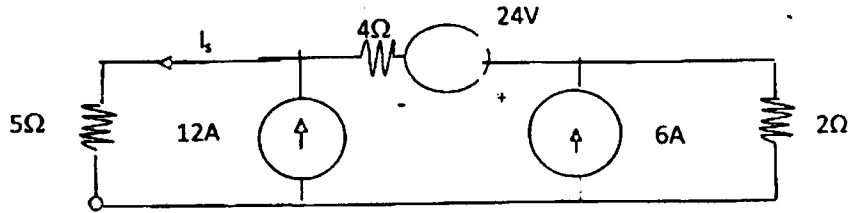

5. (a) The RL series circuit shown in fig. has current  $i = I \sin \omega t$ . Obtain the voltage  $v$  across the two circuit elements and sketch  $v$  and  $i$  also.

8

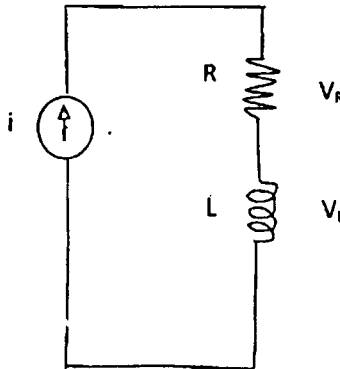

- (b) A series circuit with  $R = 5 \Omega$  and  $C = 20 \mu\text{F}$  has a current  $i = 2 \cos 5000t$  Amperes flowing through the circuit. Find total applied voltage  $V_T$  and the phase angle by which current leads the voltage.

7

6. (a) Explain in detail the parallel RLC circuit. Explain the overdamped and underdamped cases also.

10

- (b) A parallel LCR circuit with  $R = 1000 \Omega$ ,  $C = 0.16 \mu\text{F}$  and  $L = 1\text{H}$  has initial voltage  $V_0 = 50 \text{V}$  on the capacitor. Obtain the voltage  $v(t)$  when the switch is closed at  $t = 0$ .

5

7. (a) In a series LCR circuit consisting of  $R = 20 \Omega$ ,  $L = 50 \text{ mH}$  and  $C = 1 \mu\text{F}$ . Calculate the : 6
- (i) Resonant frequency ( $\omega_0$ )
  - (ii) Bandwidth ( $\beta$ )
  - (iii) Quality factor ( $Q_0$ ) of the resonant circuit.
- (b) Derive the quality factor for the series RLC circuit. 4
- (c) Find the power delivered from a sinusoidal voltage source with  $V_{\text{eff}} = 110 \text{ V}$  to an impedance of  $Z = 10 + j8$ . Find the power factor. 5