

This question paper contains 8 printed pages]

Your Roll No.....

5178

B.Sc. (Prog.) PHYSICAL SCIENCES/I Sem. B

Paper ELPT-101

Network Analysis

Time : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt any five questions.

All questions carry equal marks.

Use of calculator/logarithmic tables is permitted.

1. (a) Determine the average and r.m.s. value of a periodic current given by :

$$I = I_0 \sin(100\pi t) \text{ for } 0 \leq t \leq 0.01s. \quad 6$$

- (b) Explain the difference between a.c., d.c. and unidirectional current. 3

P.T.O.

- (c) Evaluate the sum of voltages given by :

$$V_1 = 120 \cos(\omega t + 60^\circ)$$

and $V_2 = 120 \sin(\omega t + 30^\circ)$. 3


- (d) Calculate the following and give answer in polar form :

$$V = (3 + 4j) (4 - j). \quad 3$$


2. (a) State and explain superposition theorem. 8

- (b) Determine current through 8Ω resistance. Does your


answer depend on the value of R ? 7

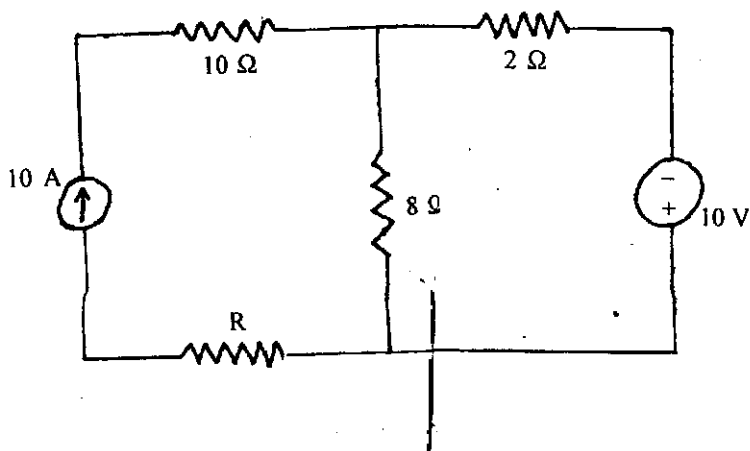

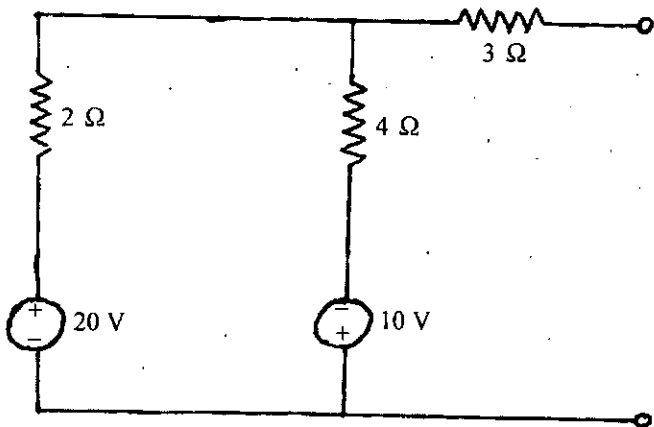
3. (a) State Thevenin's theorem. Obtain Thevenin equivalent circuit for the following network : 7



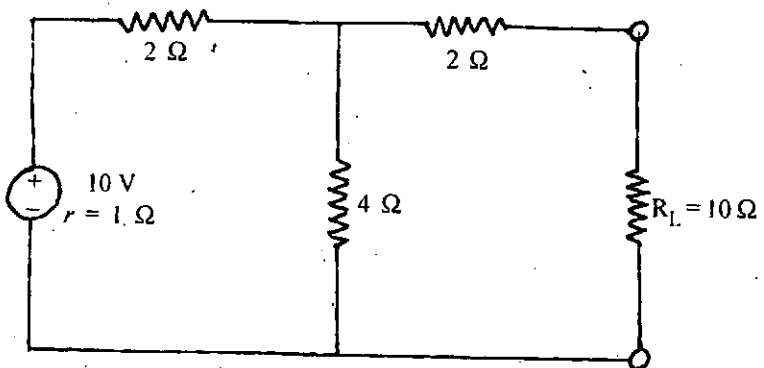
- (b) State Norton's theorem. Obtain Norton equivalent of the circuit given below and also determine current in R_L . 8



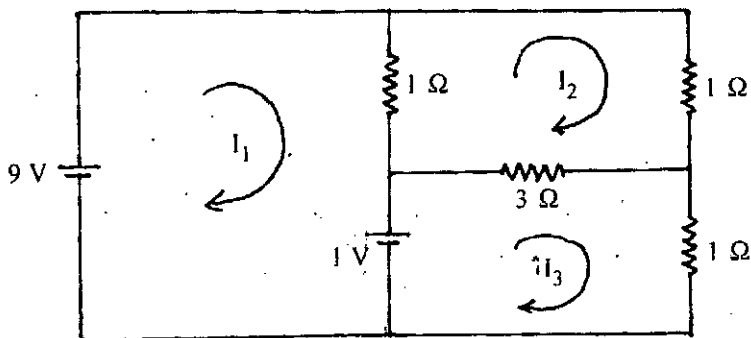4. (a) In the following circuit write mesh current equations and evaluate current in each element. Redraw a circuit with currents labelled of each element. 10




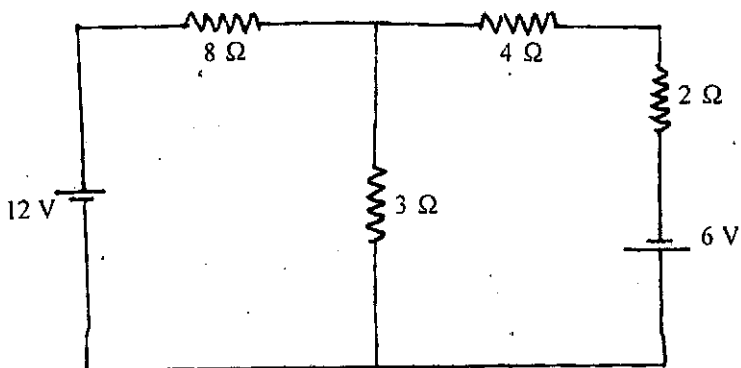- (b) For the circuit given below, write node voltage equation and determine current in each branch. 5




5. (a) What is the power loss in $10\ \Omega$ resistance in the following network ?

8

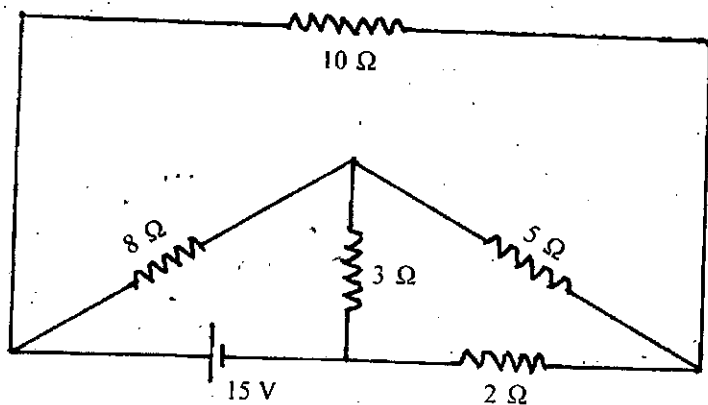


- (b) Determine direction and magnitude of current in $12\ \Omega$ resistance in the following network :

7

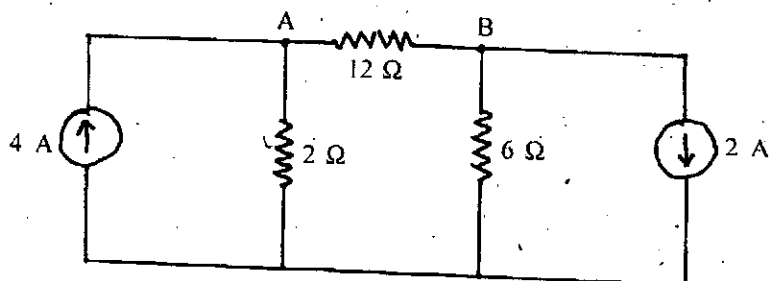

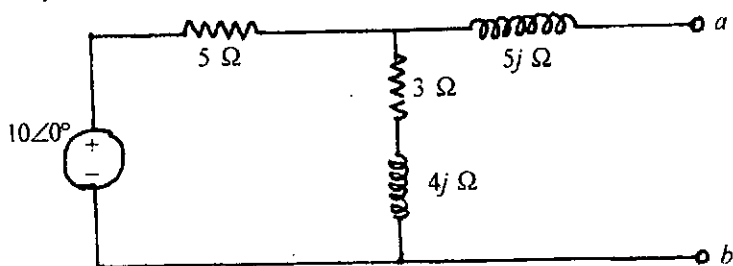6. (a) Replace the following active network at terminals a, b with a Thevenin equivalent. 7



- (b) In ideal L and C individually connected in series to an a.c. source find the expressions for current and hence show that current leads and lags the applied voltage by $\pi/2$. 4


- (c) In the following circuit identify : 4

(i) nodes

(ii) junctions

(iii) branches

(iv) meshes.

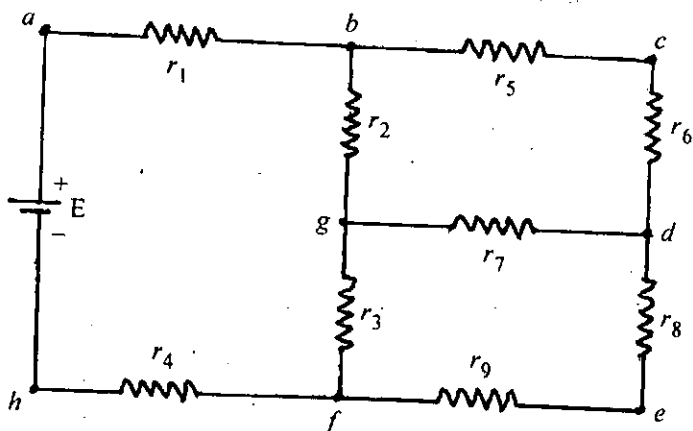

7. (a) In a series L-R circuit under transient conditions find the

expression of current under ;

10

(i) Growth of current and

(ii) Decay of current conditions.

(b) Derive the expression for energy stored in the

capacitor for an ideal series RC circuit under transient

conditions.

5

P.T.O.

8. (a) In a parallel LCR circuit with a.c. source show that minimum current flows at resonant frequency. 10
- (b) In a series RC circuit with a.c. source find the expression for current. 5