

*This question paper contains 4 printed pages.]*

**5192E**

*Your Roll No. ....*

**B.Sc. (Prog.) Physical Sciences / II Sem. B**  
**Paper ELPT-202**  
**Analog Circuits**

*Time : 3 Hours*

*Maximum Marks : 75*

*(Write your Roll No. on the top immediately  
on receipt of this question paper.)*

*Attempt five questions in all.*

*Question No. 1 is compulsory.*

1. Attempt any **five** of the following 3×5
- (a) Give one application each of a transistor in CE, CB, CC configuration.
  - (b) Define load line and quiescent point.
  - (c) State the merits of a bridge rectifier over a centre tap full wave rectifier.
  - (d) Define the three stability factors for a transistor amplifier.

[P.T.O.]

- (e) What is thermal runaway? How can it be prevented?
  - (f) Explain briefly how a transistor (BJT) can work as an amplifier.
  - (g) Sketch the frequency response of an CE amplifier and identify its bandwidth.
  - (h) Define CMRR and Slew Rate for an operational amplifier.
2. (a) Draw the block diagram of a regulated power supply and explain the function of each block in detail. 10
- (b) Explain the working of a half wave rectifier and derive the expression for its ripple factor. 5
3. (a) Explain the working of a NPN transistor describing its various current components. 10
- (b) Draw the input and output characteristics of a CE transistor and label the various regions of operation. 5

4. (a) Classify amplifiers with respect to operating point selection. 5
- (b) Explain with the help of a circuit diagram the working of a Class B push pull amplifier and obtain the expression for its efficiency. 10
5. (a) Draw a circuit diagram for a CE transistor amplifier and derive expressions for voltage and current gain and input and output impedance. 10
- (b) What is Early effect? What are the effects produced by base width modulation ? 5
6. (a) Explain the working and characteristics of an n-channel enhancement type MOSFET with the help of a well labelled diagram. 10
- (b) List the advantages of a FET over BJT. 5
7. (a) List the characteristics of an ideal operational amplifier. 5
- (b) Derive the expression of voltage gain for an inverting op-amp with a suitable diagram? 5

- (c) Draw the circuit diagram of an op-amp configured as an integrator and obtain an expression for output voltage. 5