

This question paper contains 4 printed pages.]

5193H

Your Roll No.

B.Sc. (Prog.) Physical Sciences / IV Sem. B
Paper ELPT-404
Digital Electronics

Time : 3 Hours

Maximum Marks : 75

*(Write your Roll No. on the top immediately
on receipt of this question paper.)*

*Attempt any five questions.
All questions carry equal marks.*


1. (a) Add 342 and 669 using BCD codes. 5
- (b) Add -23 and -39 using signed binary numbers.
(2's complement). 5
- (c) Convert 121.375 in to equivalent Binary. 5
2. (a) Simplify the following expression using Boolean algebra:
$$Y = \overline{\overline{ABC}} + AB + BC$$
 5

[P.T.O.]

 - (b) State duality theorem and show that the dual of an XOR is equal to its compliment. 5
- (c) Obtain the truth table of the following function and express it in sum of minterms and product of maxterms:

$$F(A, B, C, D) = \overline{B}D + \overline{A}D + BD$$
 5
3. (a) Minimize the following Boolean expression using K - map and implement it using NAND gates only.

$$F(A, B, C, D) = \sum m(0, 3, 4, 5, 7, 9, 12, 13, 14, 15)$$
 6
- (b) Implement a full - adder with two half adders and an OR gate. 3
- (c) Draw and explain the logic circuit diagram of 4-bit Adder - cum - Subtractor. 6
4. (a) Draw a logic circuit for binary to octal decoder. 7
- (b) Construct a 16x1 MUX using two 8x1 and one 2x1 MUXs. Use block diagram only. 8
5. (a) Draw the logic circuit of an edge triggered J-K flip-flop and give its truth table. If the input waveforms for J and K are as given below, find the waveform for Q output. 8



- (b) Draw the logic circuit of a Master – Slave J-K flip-flop and explain how it prevents race around condition. 7
6. (a) Draw the logic circuit of an asynchronous decade counter and explain its operation. 8
- (b) Draw a circuit for a controlled left shift register for four bits and explain its working. 7
7. (a) Draw the circuit of a 4-bit Digital to Analog Converter using R-2R ladder and explain its working. Describe as to how the accuracy of the output voltage is obtained when the input voltages for binary bits are within certain ranges. 10
- (b) Define percentage resolution of a DAC. Find the percentage resolution of a 10bit DAC which has a step size of 10 mV. 5

8. (a) Define Fan out, Propagation delay and Noise margin for logic families. 6
- (b) Draw the circuit diagrams of TTL NAND gate and CMOS NOR gate. 9