

This question paper contains 3 printed pages.

4608

Your Roll No.

B.Sc. Prog. / III

AS

PH-301 : PHYSICS

Physics of Materials & Electronics

Time : 3 hours

Maximum Marks : 75

*(Write your Roll No. on the top immediately
on receipt of this question paper.)*

***Attempt five questions in all, selecting at
least two questions from each Section.***

SECTION A

1. (a) Define Miller indices. Sketch the (100), (010) and (111) planes of a simple cubic lattice. 6
- (b) Explain the following terms :
 - (i) Primitive unit cell
 - (ii) Lattice and its basis. 4
- (c) Prove that the direct lattice is reciprocal of its own reciprocal lattice. 5

2. (a) Obtain the dispersion relation for elastic waves in a linear monoatomic chain with nearest neighbour interaction. 10
- (b) Sketch and discuss the dispersion curve. 5

P. T. O.

3. (a) Obtain Clausius-Mosotti relation between polarizability and dielectric constant of a solid. 10
(b) Draw and discuss energy band diagrams for insulators, semi-conductors and conductors. 5
4. (a) Discuss classical theory of diamagnetism and obtain the expression for magnetic susceptibility. 12
(b) Explain Meissner Effect. 3

SECTION B

5. (a) Draw the circuit diagram for a half wave rectifier and explain its working. Obtain the expressions for its (i) d.c. load current, (ii) rms load current and (iii) rectification efficiency. 10
(b) What is the difference between a positive clipper and a negative clipper? Explain with the help of circuit diagrams. 5
6. (a) With the help of a neat sketch, describe the construction of an n -channel JFET. Explain its principle of operation. 5
(b) Draw and discuss its characteristic curves. 8
(c) Give an elementary idea about MOSFET. 2
7. (a) Describe the working of R-C phase-shift oscillator with the help of the circuit diagram. 6
(b) Obtain the expression for its frequency of oscillation and the condition of oscillation. 9

8. (a) What is amplitude modulation? Show that an AM wave can be represented by a carrier and two side frequencies for each frequency of modulation. 7
- (b) Sketch the circuit of a diode detector. Explain its operation. 8