

This question paper contains 6 printed pages.

3334

Your Roll No.

B.Tech. (EC) / I J

Paper EEC-104 – NETWORKS

Time : 3 hours

Maximum Marks : 70

(Write your Roll No. on the top immediately
on receipt of this question paper.)

Answer any five questions.

All questions carry equal marks.

Assume missing data (if any).

1. (a) Differentiate between independent and dependent energy sources. Discuss the types of dependent energy sources.

(b) Find i_1 and i_2 in fig. 1.

7+7

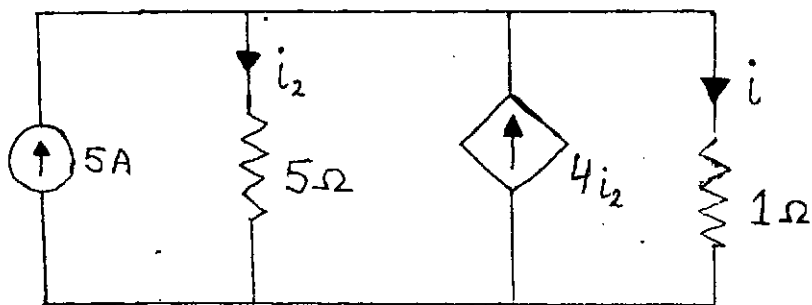


Fig.1

P. T. O.

2. (a) Find the current in the $5\ \Omega$ resistor for the circuit shown in Fig. 2 using Norton's theorem.

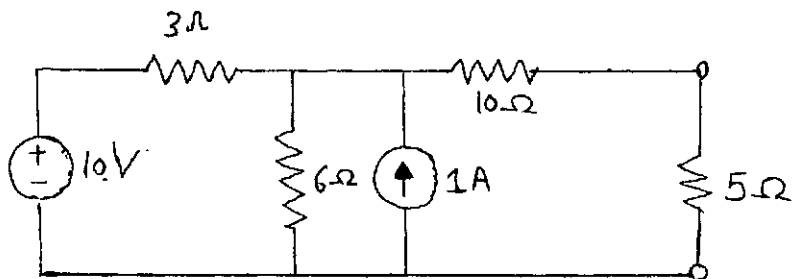


Fig. 2

- (b) Find i_0 and i from the circuit of Fig. 3 using Superposition theorem. 7+7

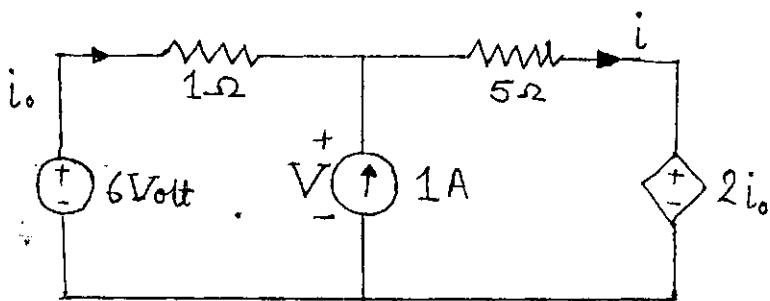


Fig. 3

3. (a) Determine the current through the $6\ \Omega$ resistor in the circuit of Fig. 4 using Thevenin's theorem.

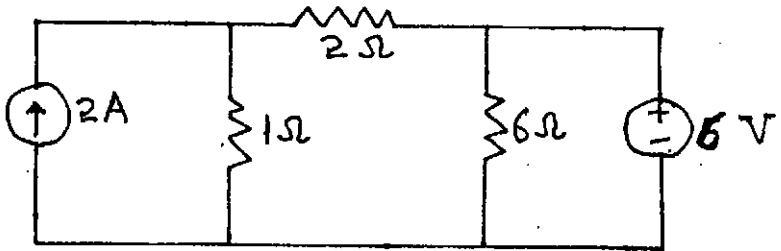


Fig. 4

- (b) Prove that the power transfer from a dc source network to a resistive network is maximum when the internal resistance of the dc source network is equal to the load resistance. 7+7
4. (a) Find the load impedance in Fig. 5 for maximum power to the load. Find the amount of maximum power.

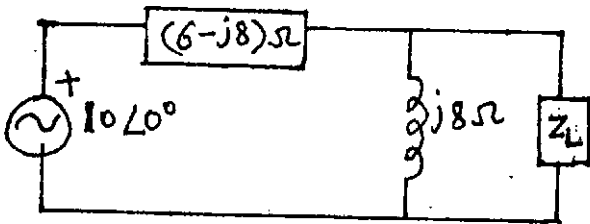


Fig. 5

- (b) In the network shown in fig. 6, $V_1=10\text{ V}$, $V_2=4\text{ V}$, $V_4=6\text{ V}$. Also $I_1=2\text{ A}$, $I_2=2\text{ A}$ and $I_3=4\text{ A}$. Check the validity of Tellegen's theorem.

7+7

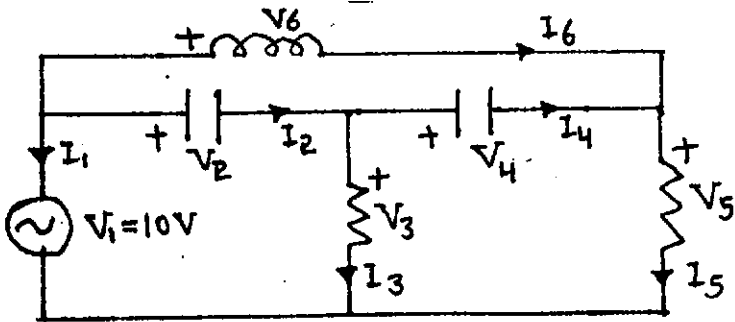


Fig. 6

5. (a) Using Nodal method, find the current through r_2 in Fig. 7.

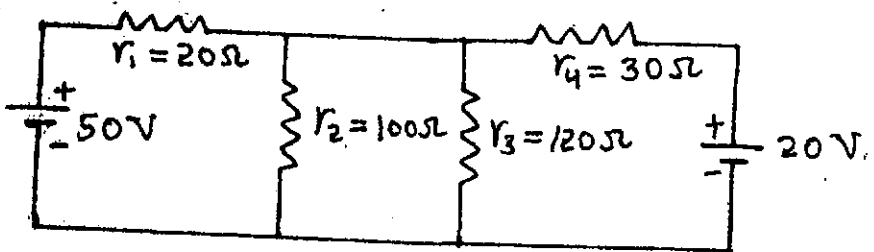


Fig. 7

(b) Find V_1 and V_2 in Fig. 8.

7+7

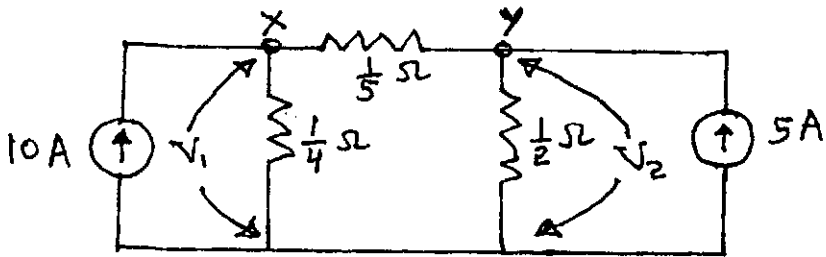


Fig. 8

6. (a) Find Z parameters of the following circuit shown in Fig. 9.

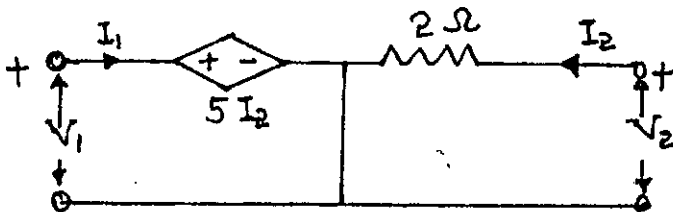


Fig. 9

(b) The Z parameters of a circuit are given by:

$$\begin{bmatrix} 4 & 1 \\ 3 & 3 \end{bmatrix}$$

Obtain the transmission parameters.

7+7

P. T. O.

7. (a) From given Z parameters, find ABCD parameters.
 (b) Find ABCD parameters in terms of h -parameters. 7+7
8. (a) State initial and final value theorem in Laplace transformation.

The current through a circuit element is $\frac{4s^2}{(s+7)}$.

Find the current in t domain as $s \rightarrow 0$ and $s \rightarrow \infty$.

- (b) In Fig. 10, the battery voltage is applied for a steady state period. Obtain the complete expression for the current after closing the switch K . Assume $R_1=1 \Omega$, $R_2=2 \Omega$, $L=1 \text{ H}$, $E=10 \text{ V}$.

7+7

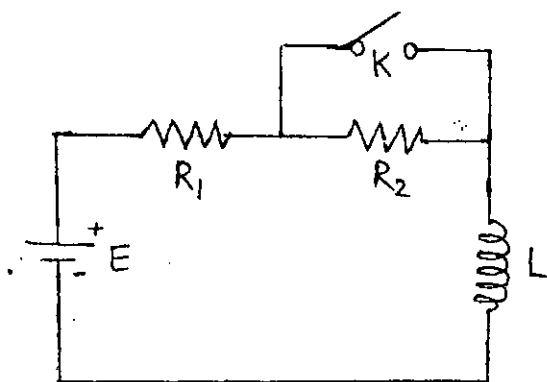


Fig.10