

8474

Your Roll No. ....

B. Tech. (E) / I

A

Paper (EEE - 104)  
NETWORKS

Time : 3 hours

Maximum Marks : 70

(Write your Roll No. on the top immediately on receipt of this question paper.)

Answer any **FIVE** questions.  
Assume missing data, if any, suitably.  
All questions carry equal marks.

1. a) Using Nodal method, find the current through  $r_g$  in Fig. 1

07

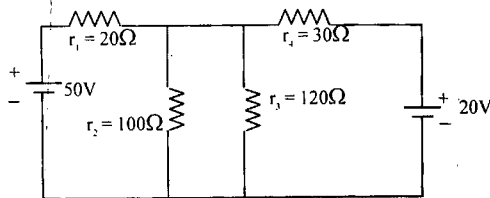


Fig. 1

- b) Find  $V_1$  and  $V_2$  in Fig. 2.

07

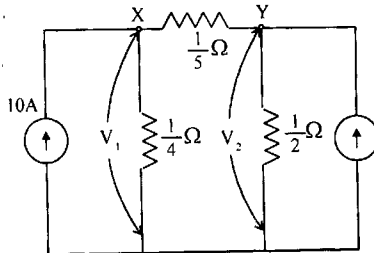


Fig. 2

2. a) Differentiate between independent and dependent energy sources. Discuss the types of dependent energy sources. 07
- b) In the circuit of Fig. 3 determine the current through the  $5\Omega$  resistor using Thevenin's theorem. 07

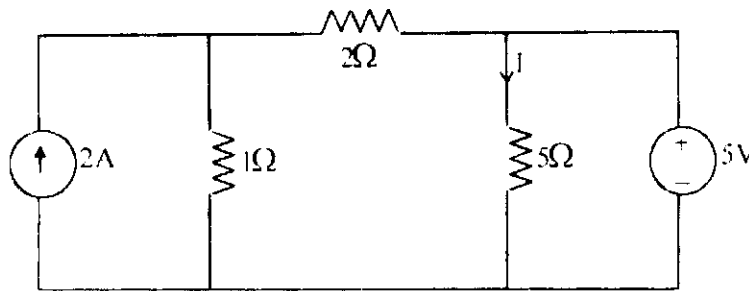


Fig. 3

- 3 a) Discuss the advantages of three phase system over single phase systems. 07
- b) Differentiate between Star and Delta connections. Derive the relationship between line and phase voltages and currents in a Star connection. 07
- 4 a) From the given  $Z$  parameters, find ABCD parameters. 07
- b) Find ABCD parameters in terms of  $h$  parameters. 07
- 5 a) In Fig.4, the battery voltage is applied for a steady state period. Obtain the complete expression for the current after closing the switch K. Assume  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $L_1 = 1H$ ,  $E = 10V$ . 07

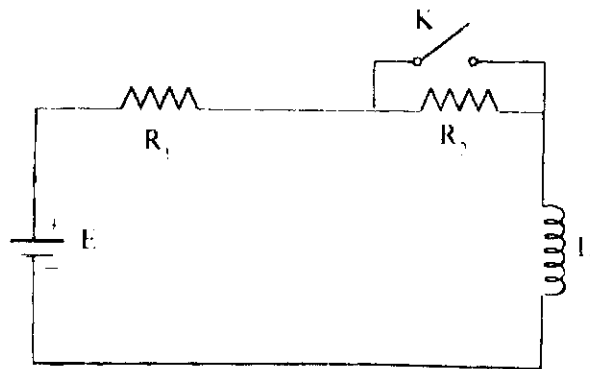


Fig. 4

- b) State initial and final value theorem in Laplace transformation. The current through a circuit element is  $\frac{4s^2}{(s^2 + 7)}$ . Find the current in  $t$  domain as  $s \rightarrow 0$  and  $s \rightarrow \infty$ . 07
- 6 a) Derive the resonance frequency of a series resonating circuit where a coil is connected across a a.c. voltage source of variable frequency. Also discuss the properties of resonance of series LRC circuit. 07
- b) A coil has a resistance of  $20\Omega$  and inductance of  $80mH$  and is connected in series with a  $100pF$  capacitor. Determine at resonance, the circuit impedance and also find the resonant frequency. 07
- 7 a) Prove that the power transfer from a dc source network to a resistive network is maximum when the internal resistance of the dc source network is equal to the load resistance. 07

- b) Explain and derive ABCD parameters of a two port network. 07
- 8 a) Discuss the constant - K band stop and constant K - band pass filters. 07
- b) State and explain Norton's theorem. 07