

This question paper contains 4+1 printed pages]

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 7992

Unique Paper Code : 2511203

F-II

Name of the Paper : Analog Devices [DC-1.4]

Name of the Course : B.Tech. (Instrumentation)

Semester : II

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Question No. 1 is compulsory.



Attempt *Five* questions in all.

Use of non-programmable scientific calculator is allowed.

1. (a) What is the intrinsic standoff ratio of UJT ? Express Mathematically. 3
- (b) Differentiate between Zener and Avalanche breakdown. 3
- (c) Calculate the value of I_C and I_E for a BJT that has $\alpha_{dc} = 0.98$ and $I_B = 150 \mu A$. 3
- (d) Draw Frequency response of CE amplifier. Why the gain of the amplifier reduces at higher frequencies ? 3


P.T.O.

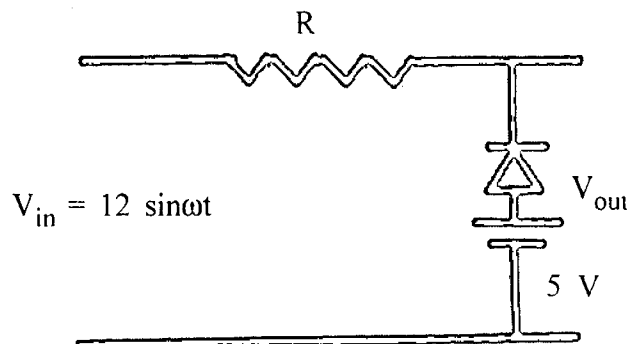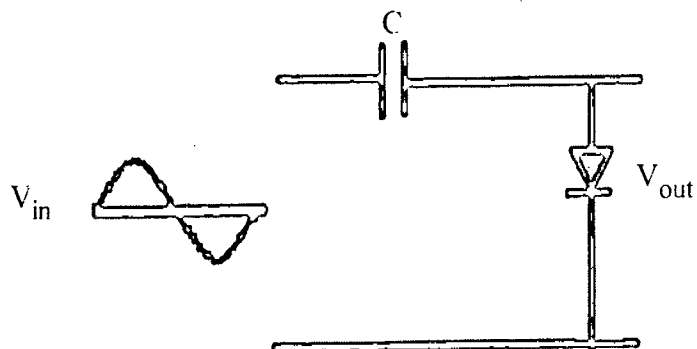- (e) A phase shift oscillator uses three identical RC sections in feedback network. Calculate the frequency of oscillation if $R = 200 \text{ K}\Omega$ and $C = 0.001 \text{ }\mu\text{F}$. Also calculate the gain of the amplifier needed for the sustained oscillations. 3
2. (a) Draw the circuit diagram of a Full Wave Bridge Rectifier and calculate :
- (i) I_{rms}
 - (ii) ripple factor
 - (iii) efficiency of rectification. 8
- (b) Sketch the output waveforms for the circuits shown below : 4



(c) Draw the block diagram of a regulated power supply. 3

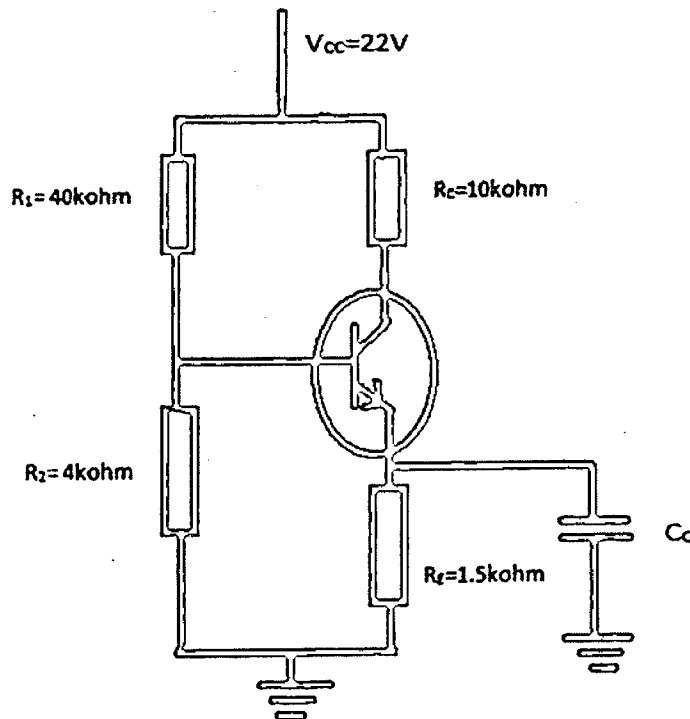3. (a) Calculate the coordinates of Q point for the following circuit. Given $\beta = 40$. 7



Does the above circuit provide stability against temperature and β variations ?

Explain.

(b) Draw an equivalent circuit of common emitter configuration using h parameters.

Calculate hybrid parameters with a.c. input open circuited having $I_b = 0$,

$V_{be} = 0.35 \text{ mV}$, $I_c = 30 \mu\text{A}$ and $V_{ce} = 2 \text{ V}$. 5


(c) Derive the relationship between input current and output current for CE transistor configuration. 3

P.T.O.

4. (a) What is Barkhausen criterion for sustained oscillations ? Draw the circuit diagram of an RC phase shift oscillator and obtain an expression for its frequency of oscillation. 8
- (b) For a class-B power amplifier using a supply of $V_{CC} = 30 \text{ V}$ and driving a load of 16Ω , determine the maximum input power and output power. 4
- (c) What is the principle of operation of a crystal oscillator ? State its any *two* applications. 3
5. (a) Explain the working of a *n*-channel junction field effect transistor (JFET). Draw its transfer characteristics. 8
- (b) Explain how UJT can be used as relaxation oscillator with suitable diagram. 4
- (c) What is the difference between the depletion and enhancement mode MOSFET ? 3
6. (a) Draw the circuit diagram of CE amplifier. Draw its ac equivalent circuit using hybrid parameters. Find out the expression for : 8
- (i) current gain
- (ii) voltage gain
- (iii) input impedance.

- (b) For the given zener diode calculate V_L , V_R , I_Z and P_Z .

4

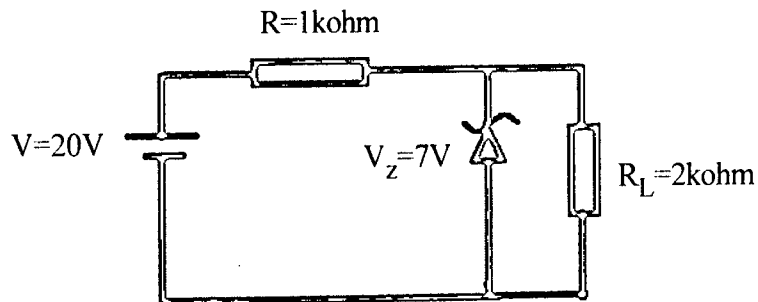

- (c) What is the ripple factor of a half wave rectifier and a center tapped full wave rectifier ?

3

7. (a) Explain the working of a p -channel depletion mode MOSFET. Also draw its output characteristics.

8

- (b) Draw the circuit diagram of a push pull amplifier.

4

- (c) Sketch the input and output characteristics for CB transistor configuration.

3