

This question paper contains 5 printed pages.

3263

Your Roll No.

B. Tech. (M) / II

J

Paper II— ELECTRONICS

(EME-202)

Time : 3 hours

Maximum Marks : 70

*(Write your Roll No. on the top immediately
on receipt of this question paper.)*

*Q. No. 1 is compulsory. Answer any four
questions from the rest.*

Assume any missing data suitably.

1. (a) Differentiate between Avalanche and Zener breakdown in diodes.
- (b) Why do you give DC bias for a transistor amplifier circuit?
- (c) Why do we prefer common collector configuration as last stage of cascaded amplifiers?
- (d) 'The input resistance of JFET is high.' Is it true or false? Justify your answer.
- (e) Explain virtual ground concept with respect to an operational amplifier.
- (f) Make a full adder using half adders and a gate. Explain its working with the help of a neat diagram.

P. T. O.

- (g) Preset and clear inputs of a flipflop are said to be asynchronous inputs. Why. $7 \times 2 = 14$

2. (a) In a full wave rectifier the voltage applied to each diode is $240 \sin 377t$, the load resistance $R_L = 2 \text{ k}\Omega$ and each diode has a forward resistance of 40Ω . Determine the following:

- (i) Peak value of current
- (ii) DC value of current
- (iii) Rms value of current
- (iv) Rectifier efficiency
- (v) Ripple factor
- (v) Output ripple frequency.

7

- (b) Draw the output waveform and transfer characteristics of the circuit shown in fig. 1. 3

 


Fig.1

- (c) The Zener diode shown in fig. 2 has a fixed voltage drop of 18 V across it so long as the Zener current is maintained between 200 mA and

2 amp. (i) Find the value of R so that the load voltage remains 18 V as input voltage is free to vary from 22 V to 28 V. (ii) Find the maximum power dissipated by the Zener diode. 4

 


Fig. 2

3. (a) With the help of a neat diagram explain the output characteristics of common emitter configuration in detail. 4
- (b) Find I_C and V_{CE} for the circuit shown in fig. 3. What happens to V_{CE} if β increases due to temperature? 7

 


Fig. 3

- (c) Explain thermal runaway and how it is removed using voltage divider biasing circuit. 3
4. (a) An n -channel JFET has $V_P = -4$ V and $I_{DSS} = 10$ mA. It is used in circuit shown in fig. 4 with $V_{DD} = +12$ V. Determine the value of R_D and R_S so that $I_D = 3$ mA and $V_{OS} = 5$ V. 7

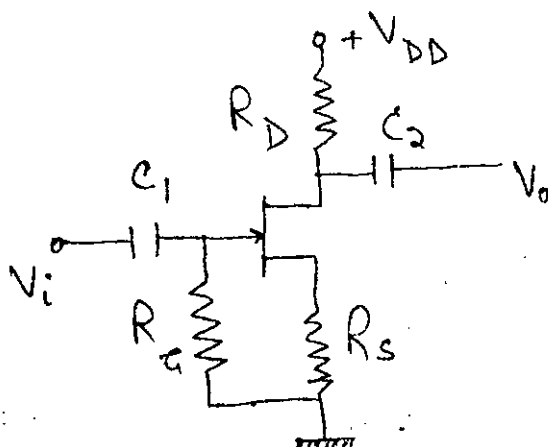


Fig. 4

- (b) Discuss the advantages of negative feedback in amplifier. 4
- (c) The voltage gain of an amplifier without feedback is 2000. Calculate the voltage gain of the amplifier if negative feedback is introduced in the circuit. Assume feedback factor as 0.01. 3
5. (a) A common emitter transistor amplifier circuit has the following characteristics: $h_{ie} = 1000 \Omega$, $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \times 10^{-6}$ A/V. If the load resistance $R_L = 10$ k Ω and source resistance is

- 100 Ω , find input resistance, output resistance, and the voltage, current and power gain. 7
- (b) With the help of a neat circuit diagram, explain the working of a Wien bridge oscillator. Derive the expression for frequency of oscillations and condition for sustained oscillations. 7
6. (a) With the help of neat diagrams explain the working of Op-Amp based integrator and differentiator. Derive the respective equations for output voltage. 7
- (b) Explain the working of a class B push-pull power amplifier. 7
7. (a) With the help of a neat diagram explain the working of a 4 input odd parity checker. 5
- (b) Minimize:

$$F(ABCD) = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$$
 5
- (c) Prove that $\overline{ABC} + \overline{BCD} + AD = AD + \overline{BC}$ 4
8. Write short notes on any two:
- (i) SCR as a full wave controlled rectifier
 - (ii) Frequency response of RC coupled amplifier
 - (iii) Working of an enhancement MOSFET
 - (iv) 555 timer. 2×7=14