

*This question paper contains 5 printed pages.*

3339

Your Roll No. ....

**B. Tech. (EC) / II**

**J**

**Paper III— ELECTRONICS**  
**(EEC-203)**

**Time : 3 hours**

**Maximum Marks : 70**

*(Write your Roll No. on the top immediately  
on receipt of this question paper.)*

*Q. No. 1 is compulsory. Answer any four  
questions from the rest.*

1. (a) What is the effect of temperature on the reverse saturation current of a diode?
- (b) Explain, how transistor can be used as a switch.
- (c) Why are MOSFETs more widely used than are the JFETs?
- (d) Mention two reasons why LC oscillators are preferred over RC oscillators at radio frequencies.
- (e) If two stages of a multistage amplifier have gains of 50 and 20, what is the dB voltage gain?
- (f) What are the drawbacks of transformer coupled amplifier?
- (g) What is the need for complementary symmetry amplifiers?

2×7=14

P. T. O.

2. (a) Draw and explain the circuit diagram of a full-wave rectifier using 2 diodes and sketch the waveforms. Derive its ripple factor and efficiency. 8
- (b) Determine  $V_o$  and  $I_D$  for the series circuit of fig. 1. 6

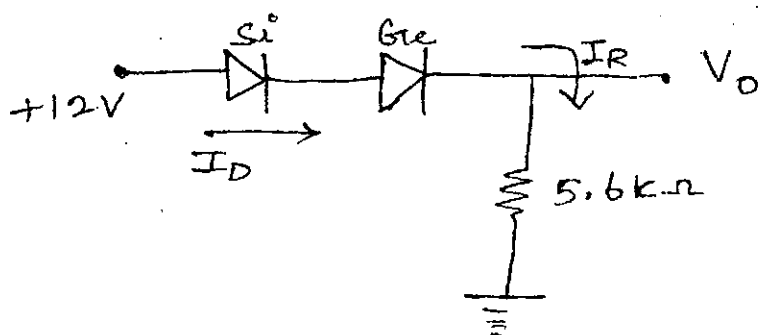


Fig. 1

3. (a) Sketch  $V_o$  for network of fig. 2 for the input shown in fig. 3.

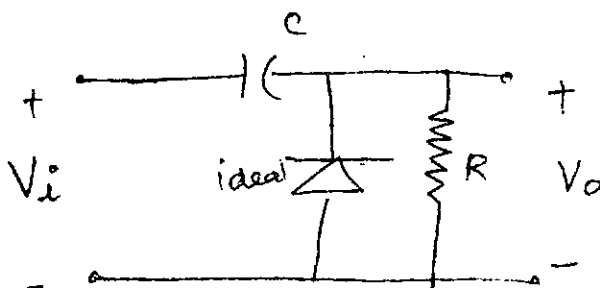


Fig. 2

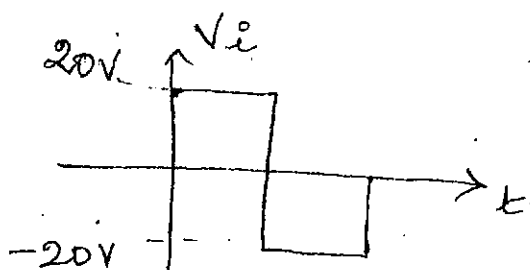


Fig. 3

- (b) Determine the range of values of  $V_i$  that will maintain the Zener diode of fig. 4 in the "ON" state.

8

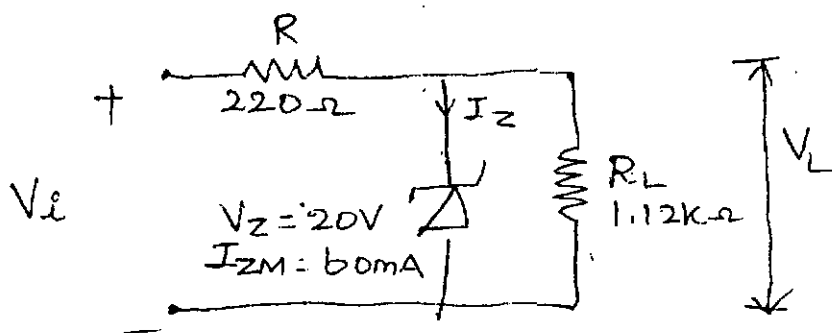


Fig. 4

4. (a) Why is biasing needed for a transistor to work as an amplifier? Explain with the help of neat diagram.

7

- (b) For the circuit shown in fig. 5 determine  $V_{GS}$ ,  $I_{DQ}$  and  $V_{DSQ}$ .

7

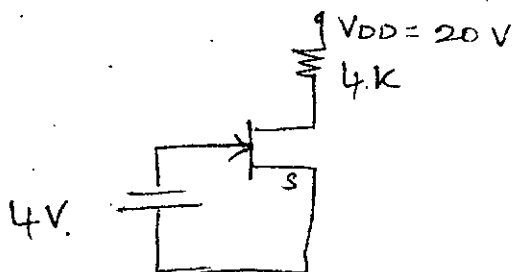


Fig. 5

5. (a) For the network of fig. 6, determine  $Z_i$ ,  $Z_o$ ,  $A_v$  and  $A_i$ .

7

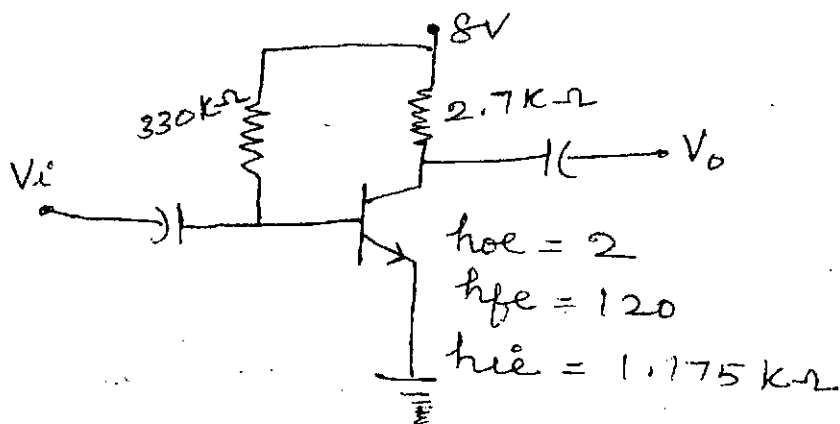


Fig. 6

- (b) Determine the voltage gain, input and output impedance with feedback for voltage series feedback having  $A = -100$ ,  $R_i = 10 \text{ k}\Omega$ ,  $R_o = 20 \text{ k}\Omega$  for feedback of  $\beta = -0.1$ .

7

6. (a) What do you mean by crossover distortion?  
Explain how it can be reduced. 7
- (b) Explain briefly the differential amplifier circuit. 7
7. (a) Explain drain and transfer characteristics of  
Depletion-mode MOSFET. 7
- (b) Draw and explain Widlar current source and  
derive the expression for it. 7
8. (a) Draw the circuit diagram of a class B push-pull  
amplifier and explain its operation. 7
- (b) Derive the conditions of oscillation of tuned  
collector oscillator with neat circuit diagram. 7