

*This question paper contains 4 printed pages.]*

**8453**

*Your Roll No. ....*

**B. Tech. (M) / II**

**A**

**Paper EME-202–ELECTRONICS**

*Time : 3 Hours*

*Maximum Marks : 70*

*(Write your Roll No. on the top immediately  
on receipt of this question paper.)*

*Question No. 1 is compulsory. Answer any **four** questions  
from the rest. Assume any missing data suitably.*

1. (a) Differentiate between Intrinsic and Extrinsic semiconductor materials. 2×7=14
- (b) Differentiate between Zener and Avalanche breakdown in a *p-n* Junction diode.
- (c) Explain recombination process in a *p-n* Junction diode.
- (d) Explain cause of drift and diffusion current in a *p-n* Junction diode.
- (e) Explain uses of clipping and clamping circuits.
- (f) What is 'Base width' modulation in BJT ?
- (g) What is Logic Gate ? Give the truth table of NAND & NOR Gate.

[P.T.O.]

2. (a) A silicon diode has reverse saturation current at  $300^{\circ}\text{K}$  is  $5\ \mu\text{A}$ . Determine the voltage to be applied across the Junction to obtain a forward current of  $50\ \text{mA}$ .
- (b) Give the diode current equation and show that this equation is valid for forward and reverse biased diode.  $7 \times 2 = 14$
3. (a) Determine the current flowing through  $1\text{K}\Omega$  resistance in the figure No. 1  $7 \times 2 = 14$

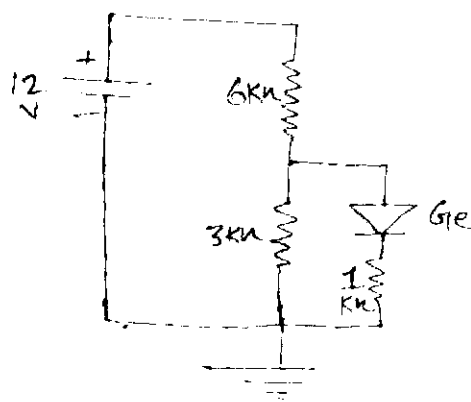


Figure No. 1

- (b) The  $p$ - $n$  Junction diode given in figure No. 2 has cut in voltage of  $0.6\text{V}$  and a forward resistance of  $150\Omega$ . If the diode can dissipate a maximum power of  $150\ \text{MW}$ , Determine the maximum permissible value of the battery voltage  $V_B$ .

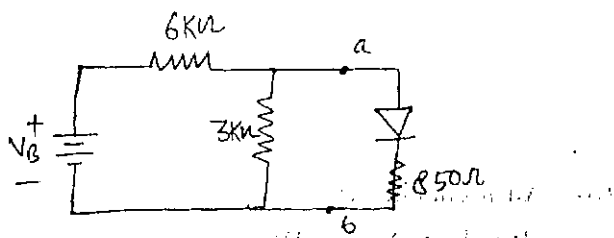


Figure No. 2

4. An AC supply of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 10:1. Determine. 2×7=14

- Im, Ide Irms
- AC power input
- DC power output
- Efficiency ( $\eta$ )
- DC voltage
- PIV
- Ripple factor

5. (a) Explain with the help of a neat diagram, the input and output characteristics of common base configuration of BJT. 4
- (b) Derive the relationship between  $\alpha$  and  $\beta$  in a BJT. 5
- (c) A Germanium transistor with  $\alpha = 0.98$  gives a reverse saturation current  $I_{co} = 10\mu A$  in common base configuration. When transistor is used in common emitter configuration with base current of  $0.22\mu A$ , determine the collector current. 5

6. (a) Explain the working principle of a Junction Field Effect Transistor (JFET). 4

(b) An n-channel JFET has  $I_{DSS} = 12 \text{ mA}$  and pinch-off voltage  $V_p = -4 \text{ V}$ . 10

(i) Determine drain current for  $V_{GS} = -2 \text{ V}$ .

(ii) If the transconductance  $g_{mo}$  of a JFET with the same  $I_{DSS}$  at  $V_{GS} = 0$  is 4 millimho, find the pinch-off voltage

7. (a) What is universal gates? And explain its uses. 4

(b) Simplify the expression 4

$$Y = AB + A\bar{B}(\bar{A}\bar{C})$$

(c) Simplify the following three variable expression using K-map method. ▲

$$Y = \sum M(1, 3, 5, 7) \quad 6$$

8. Write short notes on any two : 7×2=14

(a) Hall effect and application

(b) Power amplifiers

(c) Master-slave flip/flop.

(d) Transistor as an amplifier