

*This question paper contains 4 printed pages.]*

**8479**

*Your Roll No. ....*

**B. Tech. (EEE) / II**

**A**

**Paper-EEE-203-DIGITAL ELECTRONICS**

*Time : 3 Hours*

*Maximum Marks : 70*

*(Write your Roll No. on the top immediately  
on receipt of this question paper.)*

*Question No. 1 is compulsory. Answer any four from the  
rest. Each question carry equal marks.*

1. (a) What do you mean by edge triggered Flip-flop ?  
State the advantage of it. 2×7
- (b) What is universal logic ? Implement the truth table  
of a half subtracter using it.
- (c) State and explain De-Morgan's theorem.
- (d) Convert  $(524)_{10}$  in to Ex-3 code and binary code.
- (e) Simplify  $\overline{\overline{x} \cdot (\overline{y} + xz)} + xy$ .

[P.T.O.]

- (f) Give the voltage level range used to specify high and low logic in TTL, ECL & CMOS Logic circuits.
- (g) What is Multiplexer ? State its use.
2. (a) With neat diagram explain the operation of a serial adder. Compare with combinational adder. 7
- (b) Draw the logic circuit of a 4 bit Johnson ring counter and explain its operation and use. 7
3. (a) Design a synchronous counter, which shall count in BCD. Why this counter is known as divide by 10 counter. 10
- (b) What is the difference between a Synchronous counter and Asynchronous counter ? 4
4. (a) Give the classification of Logic families and discuss the characteristics of it. Give a comparison table for these characteristic for ECL, TTL, CMOS and PL Logic family. 10
- (b) Draw the circuit diagram of a TTL NAND Gate circuit and state the case of totem pole connection. 4

5. (a) Give the state transition table for S-R and J-K Flip Flop. How state transition take is different from Truth Table ? Does preset and clear input affects the truth table of a FF ? 7
- (b) Design a Mod-8 Asynchronous counter using S-R Flip-Flop. Show its timing diagram. 7
6. (a) With neat sketch of a RAM cell explain reading and writing operation. What is advantage of R/W memory? 7
- (b) What is PROM, & E-PROM ? Draw a diode ROM circuit which stores the sum and carry of a full-adder. The inputs of a full-adder decides the address of the ROM word. 7
7. (a) Simplify the Boolean function  $Y = \sum (m_2, m_3, m_6, m_7, m_9, m_{10}, m_{12}, m_{13}, m_{15})$ . If  $m_1$  and  $m_{14}$  are don't care terms, then what is the change in the circuit. 7
- (b) Express  $\bar{A}.C + \bar{B} \bar{C} + AB$  in canonical form. 3
- (c) Derive the truth table for the Boolean expression  $Y = (A + \bar{B})(B + \bar{C})(C + \bar{A})$  4

8. (a) Draw the circuit for a 3:8 decoder and explain its operation. 7

(b) Draw the circuit for converting three bit gray code to Binary code. Why gray code is known as reflective code ? 7