

This question paper contains 6 printed pages.

3347

Your Roll No.....

B.Tech. (EC) / III

(Part Time)

J

NETWORK ANALYSIS AND FILTER DESIGN

(EEC - 305)

Time : 3 hours

Maximum Marks :70

*(Write your Roll No. on the top immediately
on receipt of this question paper.)*

***Attempt any five questions.
All questions carry equal marks.
Assume missing data suitably.***

1. a) Show that the biquadratic function

$$F(s) = \frac{s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0}$$

is positive real if

$$a_1 b_1 \geq (\sqrt{a_0} - \sqrt{b_0})^2 \quad 05$$

- b) Synthesize the following function in both the foster forms

$$Z(s) = \frac{z(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)} \quad 06$$

- c) Test whether following polynomial is Hurwitz.

$$P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4 \quad 03$$

- 2 a) An impedance function has the pole zero pattern shown in Fig. 1. If $Z(-2) = 3$. Synthesize the impedance in a one Foster form and one Caver form. 08

P.T.O

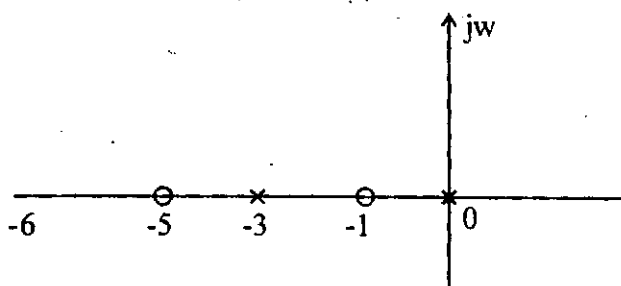


Fig. 1

- b) Describe the properties of RL impedance function. Synthesize the impedance function.

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)} \text{ in one Foster form.} \quad 06$$

- 3 a) Consider a double terminated lattice as shown in Fig 2. Show that under constant resistance condition, the voltage ratio.

$$\frac{V_2}{V_1} = \frac{1}{2} \frac{(R - Z_a)}{(R + Z_a)} \quad 05$$

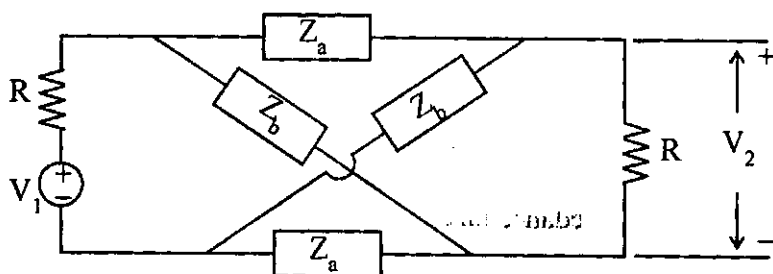


Fig. 2

- b) Synthesize the voltage ratio

$$\frac{V_2}{V_1} = \frac{(s+2)(s+4)}{(s+3)(3s+4)}$$

in terms of two constant - resistance bridged T circuits connected in tandem. 05

- c) Obtain expression for the voltage ratio V_2/V_1 for the circuit shown in Fig 3. Where does this circuit find its applications? 04

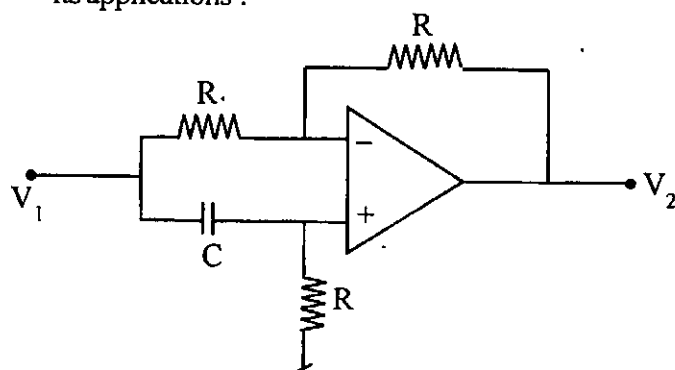


Fig. 3

- 4 a) Draw a normal tree of the network shown in Fig. 4. Write the normal form state equations. 04

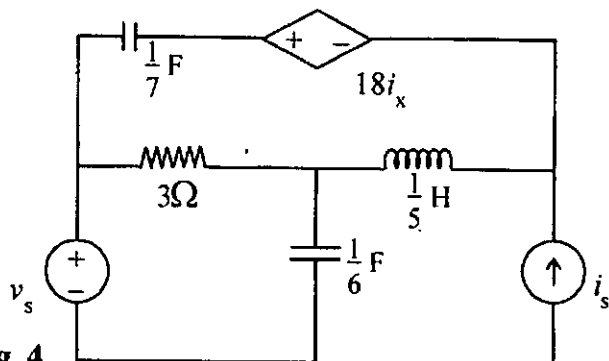


Fig. 4

P.T.O.

- b) The specification for a Butterworth band pass filter are:

$$\alpha_p \leq 3.0\text{dB for } 50\text{k rad} < \omega < 72\text{k rad}$$

$$\alpha_s \geq 40\text{dB for } \omega < 30\text{k rad}; \omega > 120\text{k rad}$$

Find its transfer function.

10

- 5 a) Design a second order Butterworth low pass filter with a corner frequency at 100rad/s and a voltage gain magnitude of 2 at zero frequency.

06

- b) In the circuit of Fig 5, determine the transfer functions

$$H_1(s) = \frac{V_0}{V_i} \text{ and } H_2(s) = \frac{V_1}{V_i}$$

and classify each as low pass or bandpass filter.

08

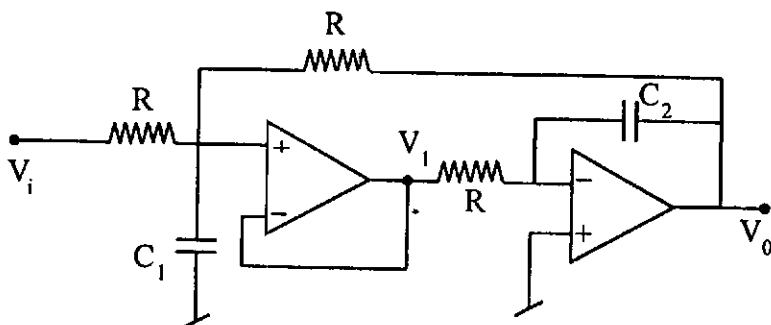


Fig. 5

- 6 a) Obtain expression for transfer function of a second order sallen - key band pass filter.

05

- b) Show that circuits given in fig 6(a) and fig 6(b) are equivalent.

09

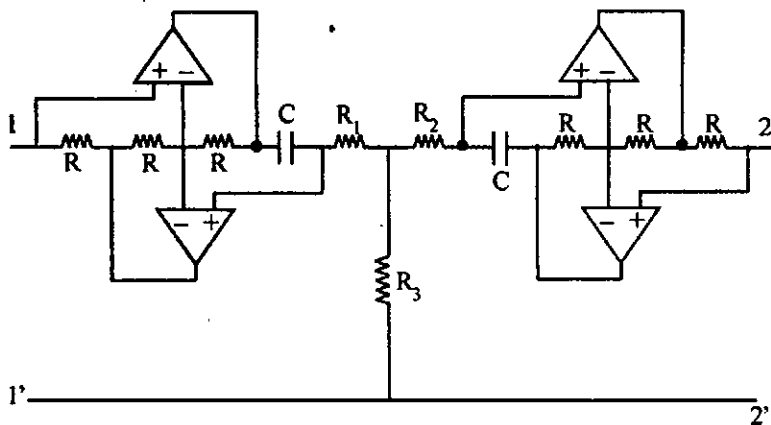


Fig. 6(a)

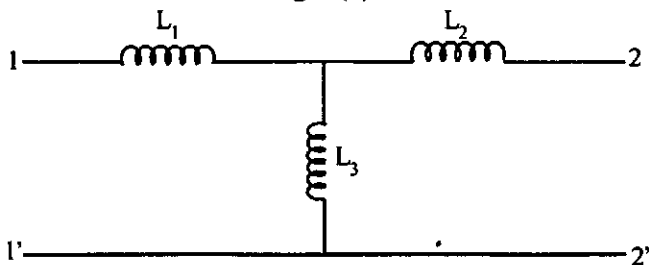


Fig. 6(b)

- 7 a) Show that the Tow - Thomas Biquad circuit shown in fig. 7 realizes low pass and band pass responses simultaneously. 09

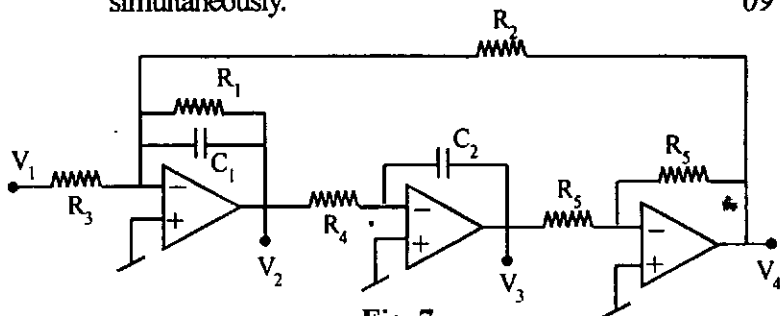


Fig. 7

P.T.O.

- b) Find the input impedance for the circuit shown in fig 8. 05

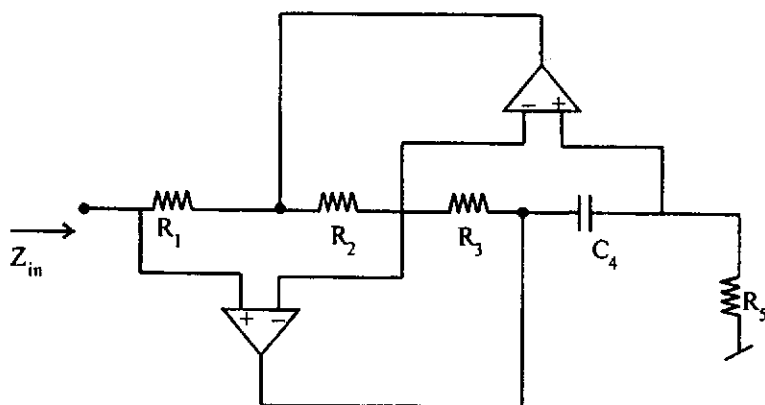


Fig. 8