

This question paper contains 3 printed pages]

Roll No.

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

S. No. of Question Paper : 1532-E

Unique Paper Code : 1143703

3-7

Name of the Paper : Basic Electronics

Name of the Course : B.Tech. Polymer Science—Allied Course

Semester : VII

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt Five questions in all.

Non-programmable Scientific calculator is allowed.

Question No. 1 is compulsory.


All questions carry equal marks.

1. (a) Explain the mechanism of formation of space charge region in a p-n junction. 3
- (b) Draw and explain the I-V characteristics of SCR. 3
- (c) Define pinch-off voltage and transconductance of JFET. 3
- (d) Convert the binary number $(1001.00102)_2$ to decimal. 3
- (e) Write the truth table for R-S flip-flop and J-K flip-flop. 3
2. (a) Explain the working of full wave rectifier. How a parallel C-filter can improve the output of a full wave rectifier ? 8

P.T.O.

(b) Draw the output waveforms of the following circuits :

5

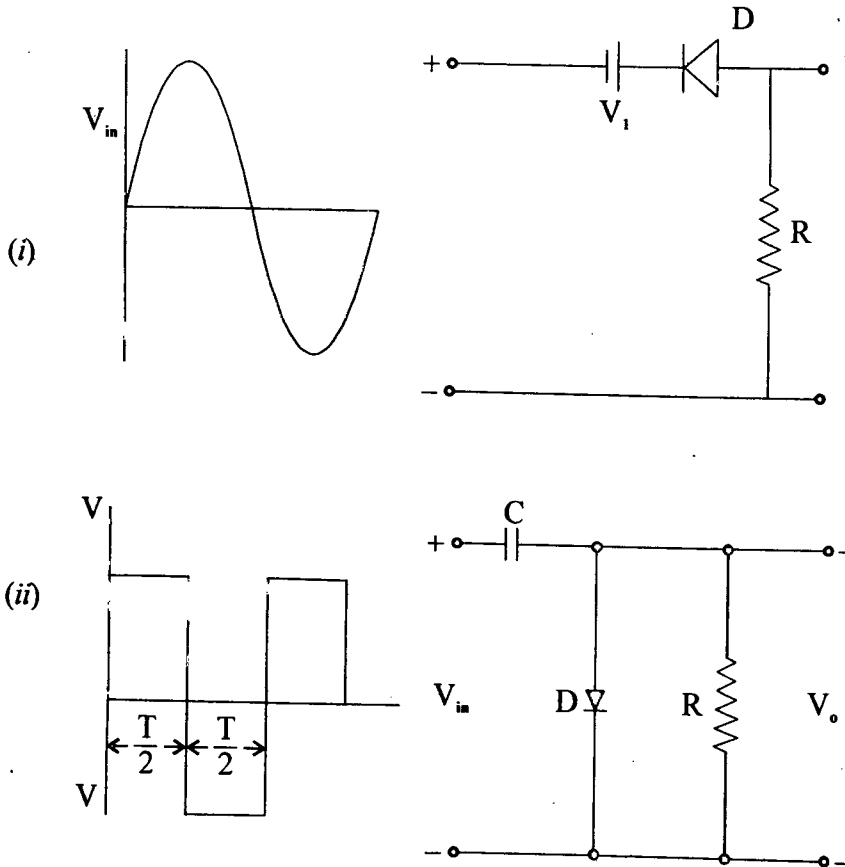

(c) Draw and explain the I-V characteristics of Zener diode.

2

3. (a) Draw and explain the input and output characteristics of a npn transistor in common emitter configuration.

7

(b) Define α and β for a transistor and drive the relation between them.

4

(c) Draw the equivalent circuit of UJT and explain its emitter characteristics.

4

4. (a) Draw and explain the transfer and drain characteristics of JFET.

6

(b) Explain the working of enhancement type MOSFET.

5

(c) Compare properties of BJT and FET.

4

5. (a) Explain a technique which converts an analog signal to a digital signal. 7
- (b) Give the truth table of Half-Adder and sketch a circuit which may be used to realize the Half-Adder. 5
- (c) What is the significance of multiplexing ? Draw and explain the circuit of a 4×1 multiplexer. 3
6. (a) Describe the working of light emitting diode (LED). 6
- (b) Explain the significance of Amplification in Electronics. 5
- (c) What do you mean by universal gates ? Implement AND, OR and NOT gate using a universal gate. 4
7. Write short notes on :
- (a) FAN-IN, FAN-OUT and NOISE MARGIN. 5
- (b) Zener diode voltage regulator 5
- (c) Complimentary MOS (CMOS). 5