

This question paper contains 2 printed pages.

Your Roll No.

Sl. No. of Ques. Paper : 1493

F-7

Unique Paper Code : 2511701

Name of Paper : EL-DC-I-701, Power Electronics

Name of Course : B.Tech. Electronics (Erstwhile FYUP)

Semester : VII

Duration : 3 hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt five questions in all. Question No. 1 is compulsory.

Use of Scientific Calculator is allowed.

1. (a) Differentiate between $p-n$ junction and power diode. 3
(b) Draw the I-V characteristics of TRIAC. 3
(c) Explain the principle of operation of chopper circuit. 3
(d) What is commutation? Why is it required? 3
(e) Define the forward blocking voltage and reverse blocking voltage of SCR. 3
2. (a) Explain the different trigger methods of Thyristors. 5
(b) Explain the recursive recovery of power diodes. 5
(c) Draw the GTO structure and explain its working. 5
3. (a) Explain the basic structure and I-V characteristics of IGBT. 5
(b) Explain with suitable waveforms the single phase bridge rectification for inductive load. 5
(c) Explain the switching characteristics of SCR. 5
4. (a) Explain the auxiliary commutation circuit with suitable waveforms. 5
(b) For class D commutation with SCR turnoff time of $30 \mu\text{sec}$, applied bias 50 V and maximum load handling of 50 A, compute the commutating components values. 5
(c) Explain the working of parallel inverter. 5
5. (a) Explain the working of Morgan chopper. 5
(b) Compute the values of Jones chopper's commutating capacitor C and transformer inductor L_1 and L_2 for the following data:
 $E_{dc} = 60 \text{ V}, t_q = 20 \mu\text{s}$
 $I_{om} = 140 \text{ A}, g = 4$
(c) If the triggering frequency of SCR is 1 kHz and turnoff time is 0.6 msec, draw the output waveform if the applied bias is 25 V. Also find the average output voltage. 5

P.T.O.

6. (a) Calculate the average and RMS value of output of phase controlled half wave rectifier with input sinusoidal signal ($e = 50 \sin 50\pi t$) at a firing angle of 30° . 5
- (b) Explain the working of continuous mode in three phase half controlled rectifiers. 5
- (c) Explain the freewheeling diode effect and its application in phase controlled rectifiers. 5
7. (a) What are the demerits of the series inverter? How can they be rectified? 5
- (b) Explain the advantages of IGBT over SCR. 5
- (c) Explain the working type B chopper circuit. 5